

# NEHRU COLLEGE OF ENGINEERING AND RESEARCH CENTRE (NAAC Accredited)



(Approved by AICTE, Affiliated to APJ Abdul Kalam Technological University, Kerala)

## DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

### **COURSE MATERIAL**



### **EET 201 CIRCUITS AND NETWORKS**

### VISION OF THE INSTITUTION

To mould true citizens who are millennium leaders and catalysts of change through excellence in education.

### MISSION OF THE INSTITUTION

**NCERC** is committed to transform itself into a center of excellence in Learning and Research in Engineering and Frontier Technology and to impart quality education to mould technically competent citizens with moral integrity, social commitment and ethical values.

We intend to facilitate our students to assimilate the latest technological know-how and to

imbibe discipline, culture and spiritually, and to mould them in to technological giants, dedicated research scientists and intellectual leaders of the country who can spread the beams of light and happiness among the poor and the underprivileged.

### ABOUT DEPARTMENT

- ♦ Established in: 2004
- Course offered: B.Tech Electrical and Electronics Engineering
- ♦ Approved by AICTE New Delhi and Accredited by NAAC
- ♦ Affiliated to the University of Dr. A P J Abdul Kalam Technological University.

### DEPARTMENT VISION

To excel in technical education and research in the field of Electrical & Electronics Engineering by imparting innovative engineering theories, concepts and practices to improve the production and utilization of power and energy for the betterment of the Nation.

### **DEPARTMENT MISSION**

- ➤ To offer quality education in Electrical and Electronics Engineering and prepare the students for professional career and higher studies.
- ➤ To create research collaboration with industries for gaining knowledge about real-time problems.
- > To prepare students with sound technical knowledge.
- > To make students socially responsible.

### PROGRAMME EDUCATIONAL OBJECTIVES

I. Graduates shall have the ability to work in multidisciplinary environment with good professional and commitment.

- II. Graduates shall have the ability to solve the complex engineering problems by applying electrical, mechanical, electronics and computer knowledge and engage in lifelong learning in their profession.
- III. Graduates shall have the ability to lead and contribute in a team with entrepreneur skills, professional, social and ethical responsibilities.
- IV. Graduates shall have ability to acquire scientific and engineering fundamentals necessary for higher studies and research.

### PROGRAM OUTCOMES

After the successful completion of the Couse, B.Tech. Electrical and Electronics Engineering, Graduates can able to acquire

- 1. **Engineering knowledge**: Apply the knowledge of mathematics, science, engineering fundamentals, and an engineering specialization to the solution of complex engineering problems.
- 2. **Problem analysis**: Identify, formulate, review research literature, and analyze complex engineering problems reaching substantiated conclusions using first principles of mathematics, natural sciences, and engineering sciences.
- 3. Design/development of solutions: Design solutions for complex engineering problems and design system components or processes that meet the specified needs with appropriate consideration for the public health and safety, and the cultural, societal, and environmental considerations.
- 4. **Conduct investigations of complex problems**: Use research-based knowledge and research methods including design of experiments, analysis and interpretation of data, and synthesis of the information to

provide valid conclusions.

- Modern tool usage: Create, select, and apply appropriate techniques, resources, and modern engineering and IT tools including prediction and modeling to complex engineering activities with an understanding of the limitations.
- 6. **The engineer and society**: Apply reasoning informed by the contextual knowledge to assess societal, health, safety, legal and cultural issues and the consequent responsibilities relevant to the professional engineering practice.
- 7. **Environment and sustainability**: Understand the impact of the professional engineering solutions in societal and environmental contexts, and demonstrate the knowledge of, and need for sustainable development.
- 8. **Ethics**: Apply ethical principles and commit to professional ethics and responsibilities and norms of the engineering practice.
- 9. **Individual and team work**: Function effectively as an individual, and as a member or leader in diverse teams, and in multidisciplinary settings.
- 10. **Communication**: Communicate effectively on complex engineering activities with the engineering community and with society at large, such as, being able to comprehend and write effective reports and design documentation, make effective presentations, and give and receive clear instructions.
  - 11. **Project management and finance**: Demonstrate knowledge and understanding of the engineering and management principles and apply these to one's own work, as a member and leader in a team, to manage projects and in multidisciplinary environments.

12. **Life-long learning**: Recognize the need for, and have the preparation and ability to engage in independent and life-long learning in the broadest context of technological change.

### **Program Specific Outcomes (PSO)**

- 1. Apply Science, Engineering, Mathematics through differential and Integral Calculus, Complex Variables to solve Electrical Engineering Problems.
- 2. Demonstrate proficiency in the use of software and hardware to be required to practice electrical engineering profession.
- 3. Able to apply the knowledge of Ethical and Management principles required to work in a team as well as to lead a team.

### **COURSE OUTCOME**

### After the completion of the course the student will be able to

CO 1	Apply circuit theorems to simplify and solve complex DC and AC electric networks.
CO 2	Analyse dynamic DC and AC circuits and develop the complete response to excitations.
CO 3	Solve dynamic circuits by applying transformation to s-domain.
CO 4	Analyse three-phase networks in Y and $\Delta$ configurations. Solve series /parallel resonant circuits.
CO 5	Develop the representation of two-port networks using network parameters and analyse.

### CO VS PO'S AND PSO'S MAPPING

CO	PO1	PO2	PO	PO	PO5	PO6	PO7	PO8	PO9	PO10	PO11	P	P	PS	PS
			3	4								О	S0	02	03
												12	1		
CO 1	3	3	3	3	3	2	-	-	-	-	2	2	3	3	-
CO 2	3	3	3	3	3	2	-	-	-	-	2	2	3	3	-
CO 3	3	3	3	3	3	2	-	-	-	-	2	2	3	3	-
CO 4	3	3	3	3	3	2	-	-	-	-	2	2	3	3	-
CO 5	3	3	3	3	3	2	-	-	-	-	2	2	3	3	-

Note: H-Highly correlated=3, M-Medium correlated=2, L-Less correlated=1

### **SYLLABUS**

### Module 1

**Circuit theorems:** DC and Sinusoidal steady state analysis of circuits with dependent and independent sources applying Superposition principle, Source transformation, Thevenin's, Norton's and Maximum Power Transfer theorems - Reciprocity theorem.

### Module 2

Analysis of first and second order dynamic circuits: Formulation of dynamic equations of RL, RC and RLC series and parallel networks with dc excitation and initial conditions and complete solution using Laplace Transforms - Time constant - Complete solution of RL, RC and RLC circuits with sinusoidal excitation using Laplace Transforms – Damping ratio – Over damped, under damped, critically damped and undamped RLC networks.

### Module 3

**Transformed circuits in s-domain:** Transform impedance/admittance of R, L and C - Mesh analysis and node analysis of transformed circuits in s-domain. Transfer Function representation – Poles and zeros.

**Analysis of Coupled Circuits:** – Dot polarity convention – Sinusoidal steady state analysis of coupled circuits - Linear Transformer as a coupled circuit - Analysis of coupled circuits in s-domain.

### **Module 4**

Three phase networks and resonance: Complex Power in sinusoidal steady state. Steady state analysis of three-phase three-wire and four-wire unbalanced Y circuits, Unbalanced Delta circuit, Neutral shift.

Resonance in Series and Parallel RLC circuits – Quality factor – Bandwidth – Impedance Vs Frequency, Admittance Vs Frequency, Phase angle Vs frequency for series resonant circuit.

### Module 5

**Two port networks**: Driving point and transfer functions – Z, Y, h and T parameters - Conditions for symmetry & reciprocity – relationship between parameter sets – interconnections of two port networks (series, parallel and cascade) —  $T-\pi$  transformation.

### **QUESTION BANK**

Sl.No	Questions	KL/COL
1	Evaluate V <sub>o</sub> in the following circuit and hence verify	K5/CO1
	Reciprocity Theorem.	
	2.0.= \$4.0.	
	2290AC 1223 7-142 Vo	
2	Using Norton Theorem, determine the current flowing	K3/CO1
	through 5 ohm resistor in the circuit shown in figure.	

	BOA (1) 5-Ω ₹ 5-Ω ₹ 1-Ω ₹ 1-Ω	
3	In a series RL circuit, the source voltage is $V(t) = 50 \sin 250t \ V$ , R= 25 ohm and L =0.005H. Determine the transient current when the switch is closed at t=0. Assume zero initial conditions.	K3/CO2
4	In a series RLC circuit, the source voltage is $V(t) = 50  V$ , $R = 35$ ohm and $L = 0.05H$ . Determine the transient current when the switch is closed at $t = 0$ . Assume initial charge on the inductor as $3A$ and initial charge on the capacitor as $0.001C$ .	K3/CO2
5	For the given network function, draw the pole-zero plot and evaluate the stability of the system. $I(s) = 3s / ((s+1)(s+3))$	K5/CO3
6	Evaluate the transfer impedance of the given network . Calculate Voltage and Current Transfer Ratio.	K5/CO3
7	In the following circuit, verify Superposition Theorem and evaluate current through 40hm resistor. Voltage source in	K5/CO1

	loop 2 is 6 angle 10 degree volts.	
	22 342 2290A 1223 -jan Vo	
8	Using Thevenin's Theorem, evaluate the current flowing	K5/CO1
	through 5 ohm resistor in the circuit shown in figure.	
	30A ( 5.2 \$ 5.2 \$ 1.2 \$ 1.2	
9	In a series RL circuit, the source voltage is $V(t) = 20$	K3/CO2
	sin300t V, R= 18 ohm and L =0.05H. Determine the transient current when the switch is closed at t=0. Assume zero initial conditions.	
10	In a series RLC circuit, the source voltage is $V(t) = 40$ V, R= 25 ohm and L =0.08H. Evaluate the transient current when the switch is closed at t=0. Assume initial charge on the inductor as 2A and initial charge on the capacitor as 0.002C.	K5/CO2
11	For the given network function, draw the pole-zero plot and evaluate the stability of the system. $N(s) = (2s+1)  /  (4  (s^2+5s+6)  )  \text{Calculate the number of poles and zeros at infinity.}$	K5/CO3

12	Evaluate i) Vi(s) / Ii(s) ii ) Vo(s) / Ii(s) for the given network.	K5/CO3
	$i_{i}(t)$ $\downarrow$ $V_{i}$ $1\Omega$ $\downarrow$ $2H$ $\downarrow$ $3F$ $\downarrow$ $5\Omega$ $\downarrow$ $V_{c}$ $\downarrow$ $Fig. 4.11$	
13	In the following circuit, verify Norton Theorem across the terminal PQ.	K4/CO1
	$12A$ $12\Omega$ $5A$ $4\Omega$ $Q$	
14	Using Thevenin's Theorem, evaluate the current flowing through 6 ohm resistor in the circuit shown in figure.	K5/CO1
	$ \begin{array}{c ccccccccccccccccccccccccccccccccccc$	
15	In a series RL circuit, the source voltage is $V(t) = 20 \sin 300t \ V$ , R= 18 ohm and L=0.05H. Determine the transient current when the switch is closed at t=0. Assume zero initial conditions.	K3/CO2
16	In a series RLC circuit, the source voltage is $V(t) = 40 \text{ V}$ ,	K5/CO2

	R= 25 ohm and L =0.08H. Evaluate the transient current when the switch is closed at t=0. Assume initial charge on the inductor as 2A and initial charge on the capacitor as 0.002C.	
17	For the given network function, draw the pole-zero plot and evaluate the stability of the system. $N(s) = (s^2 + s + 2) / (s^3 + 3s^2 + 4s + 2)  \text{Calculate the number of poles and zeros at infinity.}$	K5/CO3
18	Evaluate i) $Vi(s) / Ii(s)$ ii ) $Vo(s) / Ii(s)$ for the given network.	K5/CO3
19	A balanced three phase source of 400 V , 50 Hz supplies an unbalanced three phase load through an line has impedance of $0.1+j0.3\Omega$ , $2+j5$ $\Omega$ and $8+j6$ $\Omega$ . Determine line voltage , phase voltage, neutral - shift voltage, wire currents (line currents ) , active power, reactive power, apparent power and power factor.	K6/CO4
20	A balanced three –phase system supplies an unbalanced delta – connected load made up of three resistors 200 ohm 400 ohm and 500 ohm and a coil having an inductance of	K6/CO4

	0.3H with negligible resistance. The line – to – line voltage is 100V and the supply frequency is 50Hz . Calculate the total power in the system and the total volt – ampere (reactive)	
21	Determine the Transmission parameters and Y parameters for the network. Check the condition for symmetry and reciprocity. $Z_{11} = 8$ ohm, $Z_{12} = 12$ ohm, $Z_{21} = 16$ ohm, $Z_{22} = 18$ ohm. Draw the equivalent circuits.	K6/CO5
22	Determine the Z parameters and h parameters for the network. Check the condition for symmetry and reciprocity. A= 3, B= 160, C= 0.05, D= 3. Draw the equivalent circuits.	K6/CO5

### CONTENT BEYOND THE SYLLABUS

Ac circuits Bource Ac power supply R, L, C L- Inductor - Henry - H C- Capacitor- Farad - F Rectangular Form = A + iB
add, sub Pobr Form = 8 /0 multiply, divide A+1B=) ~ LO Y= VA2+B2 0 = tam- (B/A) YLO => A+iB A = ~ coso B= TSIND

Impedance Z = Sum of R, 4 C

Inductive Reactance

XL= 2nfL

 $\pi = 3.14$ f = frequency = 50 Hz

L = Inductor

L=XL 211f

Capacitive Reactance

Xc = 1 27fc

3 X = 5+j5 = A+jB find polar form & La Y = \( \begin{aligned} & A^2 + B^2 & = \sqrt{5^2 + 5^2} & = 7.07/ \end{aligned} \) 0 = tan - (B/A) = tan - (5/5) = 45° Ams: 7.071 /450 10 640°, find rectangular form A = YLOSB = 10 COS 40° = 7.66 B= Y sin 0 = 10 sin 400 = 6.427 7.66+j6.427 -> rectampular form. C = 4 - j3 , D = -8 + j10-1  $= 4-j^3-8+j_{10}=-4+j_{7}$ C + D = 4-j3 - (-8+j10) =4-j3+8-j10=12-j13

$$\begin{vmatrix}
20-j10 & j10 & j10 \\
j10 & 16+j2 & j2
\end{vmatrix} = \begin{vmatrix}
200200 & 5
\end{vmatrix}$$

$$(20-j10)(16+j2) - (j10 \times j10)$$

$$(320+j40-j160-j^{2}20) - (j^{2}100)$$

$$j^{2}=-1, -j^{2}=1$$

$$320-j120+20+100 = 440-j120 = D.$$
Uking Gamer's Rule
$$I_{1} = DI_{1}$$

$$DI_{1} = \begin{vmatrix}
20020^{\circ} & +j10 \\
0 & 16+j2
\end{vmatrix}$$

$$20020^{\circ} = \text{reclampular form.}$$

$$A = \gamma \cos \theta = 200$$

$$B = \gamma \sin \theta = 0$$

$$= 200+j0$$

$$DI_{1} = \begin{vmatrix} 200 + j0 \\ 0 \end{vmatrix} \qquad j \mid 0$$

$$0 \qquad | 16 + j2 \end{vmatrix}$$

$$(200)(16 + j2) - (0 \times j \mid 0)$$

$$3200 + j \mid 400 = DI_{1}$$

$$I_{1} = DI_{1} = 3200 + j \mid 400 = 3224 + 906$$

$$2440 - j \mid 220$$

$$3200 + j \mid 400$$

$$3200 + j \mid 400$$

$$7 = \sqrt{A^{2} + B^{2}} \qquad 7 = \sqrt{440^{2} + (-120^{2})}$$

$$= \sqrt{320^{2} + 400^{2}} \qquad = 456.07$$

$$= \frac{3224}{3200} \qquad = -15.255$$

$$= 7.125^{\circ}$$

$$3224.90 \mid 7.125$$

$$= \frac{90}{2} \quad 456.07 \mid -15.255$$

$$= \frac{90}{2} \quad 450.07 \mid -15.255$$

Polar form

$$I_{1} = \frac{DI_{1}}{a} = \frac{3260 + j400}{440 - j120} = \frac{3224.90}{456.07} \frac{7.125}{456.07}$$

$$= \frac{3224.90}{456.07} \frac{7.125 - (-15.255)}{456.07}$$

$$= \frac{7.071}{456.07} \frac{7.125 + 15.255}{450.255}$$

$$= \frac{7.071}{22.38^{\circ}} \frac{7.071}{450.22.38^{\circ}} \frac{6.538}{6.538}$$

$$= \frac{7.071}{22.38^{\circ}} \frac{7.071}{600.22.38^{\circ}} \frac{6.538}{6.538}$$

$$= \frac{7.071}{600.20.38^{\circ}} \frac{6.538}{600.20.38^{\circ}} \frac{6.538}{600.20.38^{\circ}}$$

$$= \frac{7.071}{600.20.38^{\circ}} \frac{6.538}{600.20.38^{\circ}} \frac{6.538}{600.20.38^{\circ}} \frac{6.538}{600.20.20.38^{\circ}} \frac{6.538}{600.20.38^{\circ}} \frac{6.538}{600.20.38^{\circ}} \frac{6.5$$

$$= (20 - j10)0 - [j10(200 + j0)]$$

$$= -(j2000 + j0)$$

$$= -j2000$$

$$I_{2} = DI_{2} = -j2000 = 2000 \angle 0^{\circ}$$

$$= -j2000 + 440 - j120 + 456 \cdot 07 \angle -15 \cdot 255$$

$$= -j2000 + 470 - j120 + 456 \cdot 07 \angle -15 \cdot 255$$

$$= -j2000 + 470 - j120 + 456 \cdot 07 \angle -15 \cdot 255$$

$$= -j2000 + 470 - j120 + 456 \cdot 07 \angle -15 \cdot 255$$

$$= -j2000 + j000 + j000 + 456 \cdot 07 \angle -15 \cdot 255$$

$$= -j2000 + j000 + j000 + 456 \cdot 07 \angle -15 \cdot 255$$

$$= -j2000 + j000 + j000 + 456 \cdot 07 \angle -15 \cdot 255$$

$$= -j2000 + j000 + j000 + j000 + 456 \cdot 07 \angle -15 \cdot 255$$


$$= -j2000 + j000 + j000 + j000 + 456 \cdot 07 \angle -15 \cdot 255$$

$$= -j2000 + j000 + j000 + 456 \cdot 07 \angle -15 \cdot 255$$

$$= -j2000 + j000 + j0000 + j000 + j0000 + j00000 + j0000 + j0000 +$$
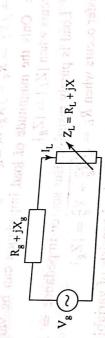
# Maximum Power transfer theorem: (AC circuits)

Maximum power is transferred to the load when the load impedance is equal to the Complex conjugate of the impedance of the network looking back at it from the load proof: Consider the circuit shown in the figure, terminals, all sources being replaced by their respective internal impedances.



# Fig. 2.187

Load current, 
$$I_L = \frac{V_g}{\sqrt{(R_g + R_L)^2 + (X_g + X)^2}}$$

Power delivered to the load =  $I_L^2 R_L = \frac{V_g^2 R_L}{(R_g + R_L)^2 + (X_g + X)^2}$  not this power to be maximum,  $\frac{\partial P_L}{\partial R_L} = 0$  and  $\frac{\partial P_L}{\partial X} = 0$ .

$$\frac{\partial P_L}{\partial X} = \frac{\left[ (R_g + R_L)^2 + (X_g + X)^2 \right] 0 - V_g^2 R_L [2(X_g + X)]}{\left[ (R_g + R_L)^2 + (X_g + X)^2 \right]^2} = 0$$

$$\Rightarrow X_g + X = 0 \Rightarrow \boxed{X = -X_g}$$

$$\therefore \frac{\partial P_L}{\partial R_L} = \begin{cases} \left[ (R_g + R_L)^2 + (X_g + X)^2 \right] - R_L 2(R_g + R_L)}{\left[ (R_g + R_L)^2 + (X_g + X)^2 \right] - R_L 2(R_g + R_L)} \right] V_g^2 = 0.$$

$$\Rightarrow (R_g + R_L)^2 + (X_g + X)^2 = 2R_L (R_g + R_L)$$

$$\Rightarrow R_g + R_L = 2R_L \Rightarrow \boxed{R_L = R_g}$$
(1)

AND STREET SAME THROUGH A THE CORD.

Mark Mark

Associated associated activities of the sounce in transferred to the page of the sounce in the page.

CAN THE SECOND COUNTY OF THE S ANTIRE AND AND THE TAXABLE OF THE TA The transfer of the winds of the importance alone is variety. The complete of the party of th

The same and the different Amenda casales

The last the inequitable of load angestance can be varied. Maximum pages

The last is justed, resistive. But source impositance  $= K_g + j X_g M_{\rm max}$ はり かんだり まとって 一分 ようし

1 日本の 1 日

Case (with Source impositance  $= R_0 + \beta N_0$  and lead coursions of variable  $R_0$  and the ON THE STATE OF THE PARTY OF TH The state of the s

Windowski process with the second of the sec

One will Source impositance is  $R_g+\mu N_g$  and lead consists of a fixed resistance k

Find the value of Zq in the circuit shown in the 2.188 for many

- Land a complete impredence with both variable real and imaginary parts



(i)  $Z_L$  is a complex impedance with both variable real and imaginary parts.

$$Z_L = 1 - j_2 \Omega$$

$$Z_L=1-j_2\Omega$$
 (Refer case ii)  $p_{\rm BBH}$  (Refer case ii) Load current  $= I_{L^2}=-\frac{\alpha}{\alpha}$ 

Load current 
$$=I_{L}=\frac{1}{(1+j2+1-j2)}=5$$
 As on a bod of the resistor.

(ii) 
$$Z_L$$
 is a pure resistor =  $R_L$ 

$$R_L = \sqrt{R_g^2 + X_g^2} = \sqrt{1^2 + 2^2} = 2.236 \,\Omega.$$
 (Refer case iv)

Load Current = 
$$I_L = \frac{10^{-001} \text{ cm}}{3.236 + j2} = \frac{2.629 \text{ A}}{2.629 \text{ A}}$$
,

Load power = 
$$P_L = I_L^2 R_L = 15.45 \text{ W}$$

Find the value of  $Z_L$  is the previous problem, for maximum power Find  $\mathbb{Z}_{L}$  in the circuit shown, for maximum power trans transfer to it, given that  $Z_L$  can be varied only in magnitude.

# Solution:

In the circuit shown in fig. 2.189 the load consists of a variable resistor and a capacitance variable between  $10 \Omega$  and  $20 \Omega$ . Find the value of  $R_L$  for maximum power transfer to the load and calculate the maximum power.

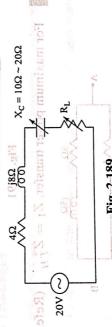


Fig. 2.189

For maximum power transferzare Solution:

$$\Omega$$
 (P21.11 – E2.14)  $Z_{LC}$ = (4 $c$ =18)  $\Omega$ -25.4 (Refer case)ii) (21 + 3) = 14.7


But since the value of load reactance can be varied only between  $10~\Omega$  to  $20~\Omega$ ,  $X_{\rm Load} =$ 

Now, 
$$R_g = 4\Omega$$
,  $X_g = j8\Omega$ ,  $X_L = -j10\Omega$ .  $2.25 - 20.02$ 

$$\Rightarrow R_L = \sqrt{R_g^2 + (X_g + X_L)^2} = \sqrt{4^2 + 2^2} = \sqrt{20} = 4.472 \,\Omega.$$
 (Refer case vi)

Load Power,  $P_L = I_L^2 R_L = 2.298^2 \times 4.472 = 23.607 \text{ W}$ 

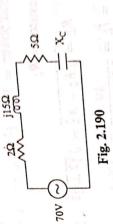Problem 4 Find the value of capacitive reactance to give maximum power o the load in the circuit shown in fig. 2.190. Also find the power



For maximum power transfer to the load,  $X_c = -j15\,\Omega$ . (Refer cases, Solution:

oad current =  $I_L = \frac{7.2}{2 + j15 + 5 - j15} = 10 \text{ A}.$ 

ower delivered to the load =  $P_L = I_L^2 R_L = 10^2 \times 5 = 500 \, \mathrm{W}$ 

Problem 5 Find  $Z_L$  in the circuit shown, for maximum power transfer and find aximum power.

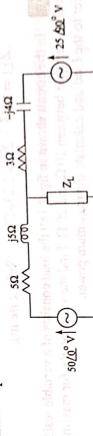


Fig. 2.191

For maximum power transfer,  $Z_1 = Z_{TH}^*$  (Refer case ii)

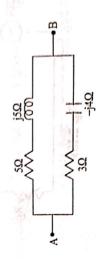



Fig. 2.192

 $Z_{TH} = (5+j5) \parallel (3-j4) = 4.385 / -15.255^{\circ} \Omega = (4.23-j1.154) \Omega$ pen circuit voltage  $(V_{AB})$ : (from fig. 2.193),

 $I = \frac{50 \, /0^{\circ} - 25 / 90^{\circ}}{1} = 6.934 \, / -33.69^{\circ} \, \text{A}$ 

their posit In a linear

Thevenin's

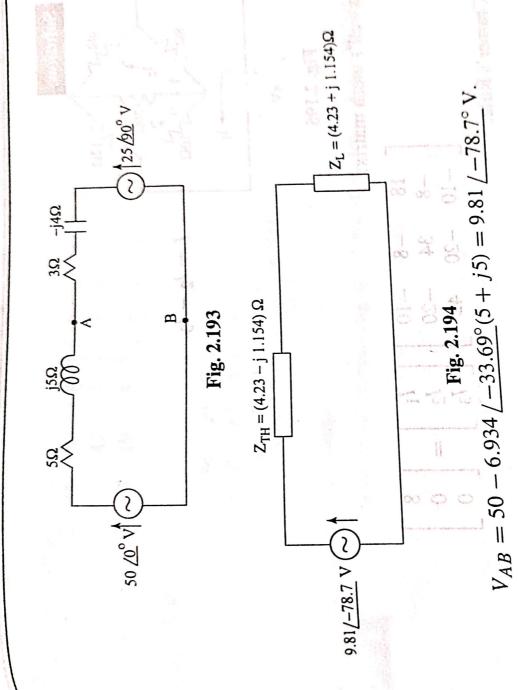

Thevenin's equivalent circuit:

s equivalent circuit: 
$$\frac{9.81 \ / - 78.7^{\circ}}{4.23 + 4.23} = 1.1596 \ / - 78.7^{\circ} A$$
Load current =  $I_L = \frac{9.81 \ / - 78.7^{\circ}}{4.23 + 4.23} = 1.1596^2 \times 4.23$ 
Power delivered to the load =  $P_L = I_L^2 R_L = 1.1596^2 \times 4.23$ 

EET201 Circuits and Networks closed loop & devices operate Ohm's Law > V=IR 丁二岁 / 尽二头 Network -> energy source and elements (R, C, L) TACTIVE -> V, I sources L) Pasnive -> R, C, L Vo Hoge source De Curent source V = AC DC AC AC ACD AC source - AC circuits DC source - DC circuits

2 DC 1+ 0 00 **T-**Resistance in Series Reff=R1+R2 +R3+... -M-W-W-2 } D  $V_1 = IR,$ Same aucent
Same aucent
Different voltage Va=IR2 Current, flows this the element Voltage appear a moss the element Kesistance in parallel Same Voltage
Different current  $\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$ 

Total current = I I, = IR2 RI+R2 I2 = IR1 RI+R2.

Source Transformation Convert V source into I source and vice Versa


V = R

Vsource in series with Resistor

I D SR

cusent source in parallel with Resistor.

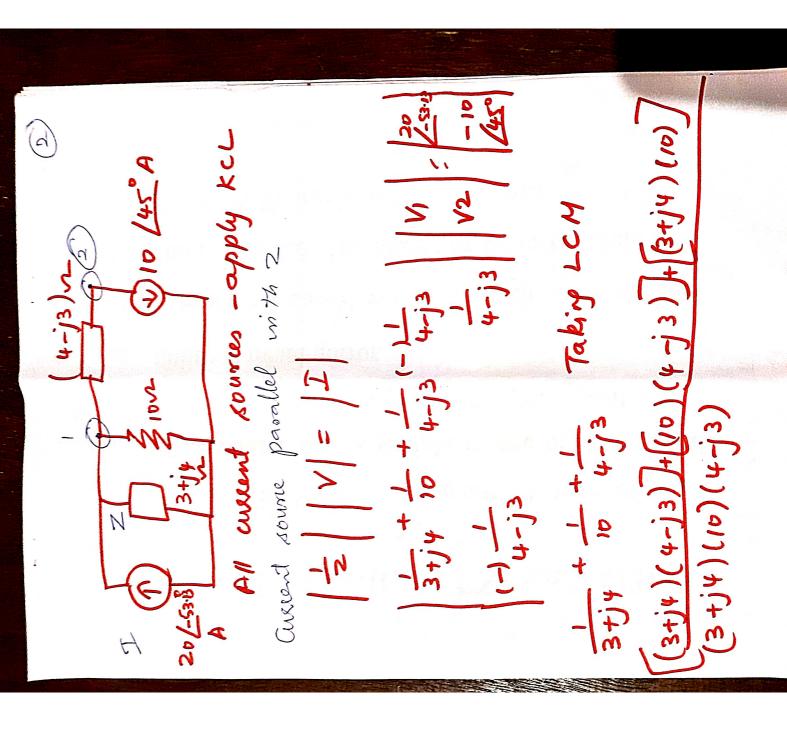KCL- Ac arount All current Kources (4-j3) v. 310v2 100 LOOV Vo Itage Source source Convert voltage source into Current source  $T = \frac{100 \angle 0}{R(2)} = \frac{100 \angle 0}{3 + j \cdot 4} = \frac{100 \angle 0}{5 \angle 53.8}$ 3+14=5/53.13 X cos Y= VA2+B2 = V32+42 = 5 0= tan-'(8/A) = tan-'(4/3) = 53.13°  $=20 \ lo-53.13 = 20 \ lo-53.13^{\circ}A.$ 



142+32 = 5 tan (-3/4) = 36.87 / 1 = 1 245° 0.2 (81.87) tan (-3/4) = 36.87 / 1 = 1 (445° = 0.2 (81.87) (415) = 5 (26.87) (245° = 0.2 (81.87) 250 [16.26 [-6.0] (12 +j7+12) + (40-j30) + (30+j40) tan-1 (20) 94 +117 = 95 42 10.25 = 0.38 V2402+702 240+170 (12-j9+j16-j22)+(40-j30) 77.91 -120-190+1160-12120 1942 +172 = 95.42 (30 fite)(4-j3) tan-1(47)=10.25 + (30+j40) + 240 +170 4111 4-13

=(0.019+j 0.074) - (-0.038+jo.61) (hc. En) ho.0) - (98.5c) 960.0)= D= 0.057 + j0.063 - rectangular from = 0.019 + 10.074 + 0.038 - 10.011 ( -0.2 x -0.2 (81.87+81.87) 20 2-53.13 D=(0.38x0.2 /-6.01+81.87)-D = 0.035 (47.86 - polar form 0.2 (81.87° -10 /45 0.38 (-6.01 - 0.2 (21.27) - 0.2 (31.37°

$$DY_{1} = \begin{vmatrix} 202 - 53.13 & -0.2 & 281.87 \\ -10/45 & 0.2 & 281.87 \end{vmatrix}$$

$$= (20\times0.2 & 2.3.73 + 81.87) - (-0.2\times-10 & 21.87 + 45)$$

$$= (4/28.74) - (2/126.87)$$

$$= (3.51+j1.92) - (-1.20+1.5j)$$

$$= 3.51+j1.92 + 1.20-j1.6$$

$$= 4.71+0.32j = 201-rectangular$$

$$= 4.751 & 3.887 = 201 = polar form.$$
By Cramerla Rule
$$V_{1} = \frac{202-53.13}{2} - \frac{202-51.86}{2} - \frac{202-51.86$$

V, = 40.22 - j 38.81 V => Reitangular 20 (-53.130 DV2 = 0.38 (-6.01 -10/450 -0.2 /81.87 =(0.38x-10 (-6.01+45) -(20x-0.2 [81.87+(-53.13)) = (-3.8 /38.99) - (-4 /28.74))  $= \frac{39.17}{=(-2.95-j\ 2.39)} - (-3.51-1.92j)$ = -2.95-j2.39+3.51+j1.92 = 0.56 - j 0.47 = DV2 = Reitangular = 0.73 [-40.006 = DV2 = Polar V2 = 0.73 (-40.006 0.085 47.86

= 8.588 [-40.006 - 47.86]  $V_2 = 8.588$  [-87.866] V = polar form  $V_2 = 0.3198 - j 8.582$  V = Rectangular form.

Kirchoff Circent Law (KCL) Total
Concert at a junction is zero
I norming concert = out going
concert in a node

' La all current sources Apply KCL, all current sources ATT ATT Identify Nodes. Node = a junction wherein two or more elements join together No. of nodes = order of matrix

eg.  $2 = 2 \times 2$ =  $3 \times 3$ Each and every element will be connected to two different nodes Select minimum no. of nodes KCL -> Nodal Voltages.

All current (2) 342 (1) 20A No. of nodes = 3 = order of matrix = 3×3 Ohm Law = Y=IR I = VIII = | | V At node/ | | | | | = | I | 911= | - + - | = 2 At node 2 922=+++++ 2.25 -+ At mode 3 931 a33 = /+ -+ -a12 = a21 = . Rubet node 1 and 2 932 = 923 = R bet pode 2 and 3

| T | V = T | b Nodal Voltage |  $\begin{vmatrix} 2 & -1 & -1 & | V_1 & | & 10 \\ -1 & 2 \cdot 25 & -1 & | V_2 & = & 0 \\ -1 & -1 & 2 & | V_3 & | & 20 \end{vmatrix}$ V<sub>1</sub> = voltage at nucle / V<sub>2</sub>, V<sub>3</sub> = V at node 2 and 3. For all common elements (912,021, a 31, a 13, a 23, a 32) put regative sign forcuseent sources 11/4-put position sign VV, É y put regative sign V, = 133.33 V

 $V_2 = 120 V$   $V_3 = 13646V$ 

KVL- 18 How Haye source 033 = S+10 +6 =21 911 = 2+2+5 = 110 922 = 6+6+3=15 93503556 921=012=6 a135 a31 55 "\ I, ] I2] => same, so -> II => Same 1 60 - 5 -> 12 => same, 10-6 (R) II/= 1V/ 356 " H アント

ohm Low 7 source transformation  $I = X, \quad V = IR$ Voltage Law: De circuit Kirchoffx of voltage drops in Algebric Rum a closed loop is zero. loop wing XVL > calculate, current
Apply XVL > circuit having voltage sources. 10n 30n Mateix Method. 20V = (1) 2.5-1 + 40 V All Voltage sources. No. of closed loop = 2 Order of matrix = 2×2 = columns No. of o closed loop = rowsder of matrix.

 $a_{11} a_{12}$  |12.5-2.5|  $|T_1|$  |20|  $|T_1|$  |25|  $|T_2|$   $|T_2|$ 0hm's low: |R| |I| = |V| |I| = |V| |I| = |I| a11 = Sum of Rim loop 1 = 10+2.5 922 = Sum of R in 60p2 = 30+2.5 912 = 921 = Common R to bop (1) and (2) = 2.5Based on loop curent direction, assign sign to common element 9,2,92, (2.52) · direction of I, and I2 are same (2, 2), use regative sign (-2.5)

Iz is leaving negative terminal of 40 V. (i. wing -40 V) from mateix, write loop equation I, is leaving positive terminal of Based on loop current learng I, = 1.375 A JZ2= -1.125A. terminal, who polarity for -2.511 + 32.5 In = -401 12.5 II - 2.5 I2 = 20 20 V. (: wing + 20 V) voltage source.

ART 1/2/= 1V/ > Dhm Law a12 = a2, = 12 943 = 938 = 2 azz= 12+1+2=152 a13=93 =0 N 84 .0order of matrix = 3×3 No. of closed borp = 3 Draw loop current II = 0.16A IZ = 0.02A I3 = Ĥ All voltage sources an 22+12= 142 93353+2F52 122 0/3 152 023 152 023 153 023

KVL- 18 How Haye source 033 = S+10 +6 =21 911 = 2+2+5 = 110 922 = 6+6+3=15 93503556 921=012=6 a135 a31 55 "\ I, ] I2] => same, so -> II => Same 1 60 - 5 -> 12 => same, 10-6 (R) II/= 1V/ 356 " H アント

Maximum Power Tramsfer Theorem. DC circuits RL= RTH. Find Re for which maximum power is transfered. Find the maa. power delivered. Step1: Find KTH Find RTH amoss AB. RTH = 2.99 2 = RL

Power delivered (power delivered by load Resistance PL: ILRL IL W 52 RL 2 42 23.33 - 20V 2.99 T2 T2 T IL is current flowing this RL Use KVL to find IL  $\begin{vmatrix} 8.33 & -3.33 & -5 \\ -3.33 & 10.32 & -4 \\ -5 & 4 & 15 \end{vmatrix} = \begin{vmatrix} 20 \\ 12 \\ 13 \end{vmatrix} = \begin{vmatrix} 20 \\ 0 \\ 0 \end{vmatrix}$ I2 = 2.33 A. = IL PL= IL RL = (2.33) (2.99) =16.23 Watt.

Norton's Theorem Find the cureent this Iva Resistor in the circuit using Norton Theorem B V 33.33n = 20 V 1. Apply Norton Theorem auons AB 2. Find Load Resintance RL=11/2 RL aurons AB. 3. Find RTH KTH = 2.992 4. Find Isc: Short circuit current through AB (Norton Terminals) Short  $T_2$ 4N  $T_3$   $T_2$   $T_3$   $T_4$   $T_2$ 4N  $T_3$   $T_4$   $T_$ Iz is flowing Thus' AB · IZ B short circuit aucent.

Using IL = Isc RTH = "4.67 x2.99 Gussent Division RTH + RL Rule = 3.5 A 6. Find current thus INR = IL A S. Draw Norton Equivalent 30 TSC (1) 2.47 & 12. 4.6719 2.47 & RL I2=4.67A = ISC H -5 -4 165 13 (V) Isc T) Isc 8.33 - 3.33 - 5 -3.33 7.33 -4 17 Iscir -ve ( If Is cis +re arcut 84 KVL

Norton Theorem - AC circuit 122 00141 10 3j42 7 - j8n 120 L450 V No Load Resistance/Impedance. No element connected between A and B AB > Norton Terminal. Step! : calculate 2 TH ZTH = 3.74 - 16.511 v 2TH = 7.51 [-60.13° 2 step 2: calculate Isc Short circuit areant the PB To 3j42 -jant Isc 120 /450 Sime no element between AE,B, All circents will flow this' AB.


Resistance Dopedome in As path u zero. parallel combination - 1842 and Als is Zew -18+0 120/4° II, 3/4" IZ V Isc = I2 : calculate I2, use KVL 121 11 = 1V1 => (2x2) mahr 6+j4 -j4 | I) = 120 245 | -j4 12+j8 | I2 | = 0 D=((6+j4)(12+j8)) - (-j4x-j4) =(72+j48+j48+j32)-(j216)

02 1562 +11. 111 = (36) - mot 296+2951 =0 = ((+j4)0 - (-j4(84.85+j84.85)) 120 /45° = 120 cas 45° + 1 120 81 n45° = J339.42 + 339.42 ton" (339.4) = 46 +195 = 91+96+04 = 012 = 6+j4 84.85+184.85 = 1339.4-339.4 = DIZ = - (-) 339.4 - 12339.4) - (-) 339.4 + 339.4) 022= 16+j4 120 C450 = (75+196-32)-(-16) 7-339.4 +1 339.4 784.85 + 184.85

72 = 072 = 479.98 /-45° = 4.32 /- 104.74° A = 4.32 /- 104.74° A

= 4.32 (85) (-104.74) + j 4.32 Sin (-104.74) = -1.099-j 4.178 A T2= Isc.

step 3: Draw Northern Egmi valent armit

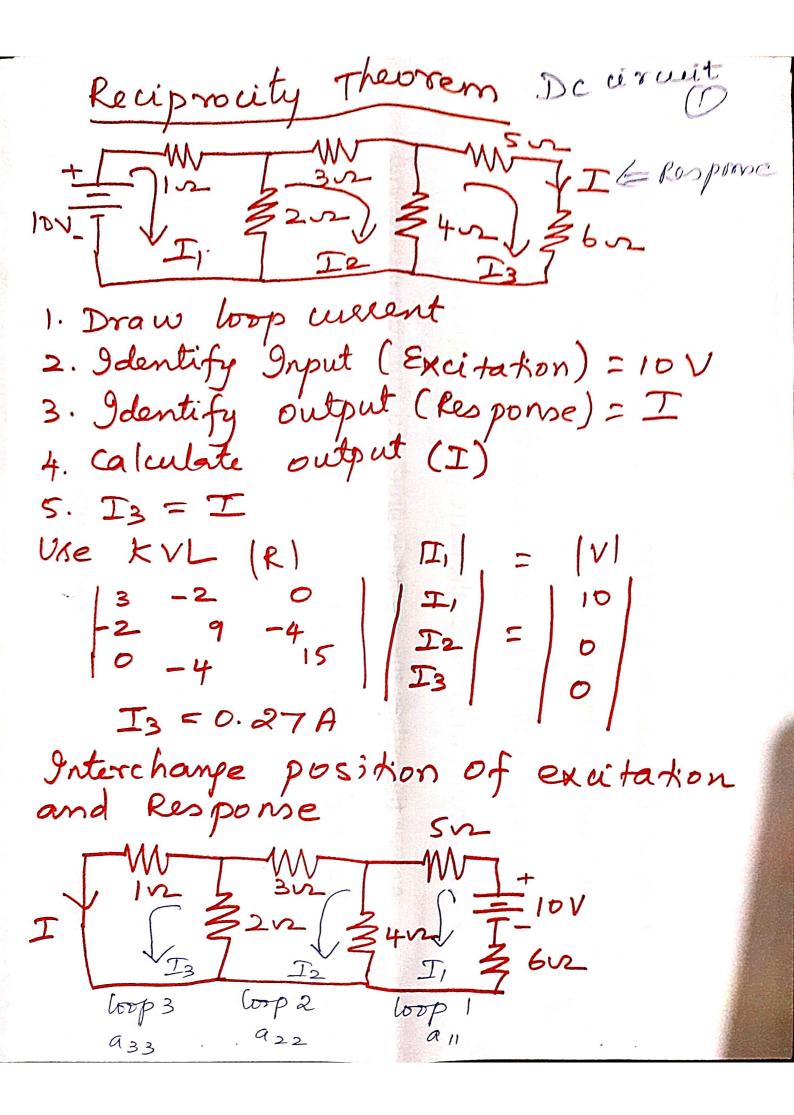

9 put = 10 V, o/p = I = I3 use KVL  $\begin{vmatrix} 15 & -4 & 0 \\ -4 & 9 & -2 \\ 0 & -2 & 3 \end{vmatrix} = \begin{vmatrix} 10 \\ 12 \\ 0 \end{vmatrix}$  $I_3 = 0.27 A$ If we interchange the position of excitation and response, we will get same answers.

100 Lo V Draw loop currents based on 100 Lov Three loop cureents = Three closed loops = (3x3) matrix (R)

(a) Same loop cureents direction

(b) III(c) Same loop cureents direction

(c) III(d) IIII(e) Same loop

(f) IIII(f) IIIII(f) IIIIII(f) IIIIIIII(game loop)

(game loop

(game l  $0 | I_1 | 100 L0^{\circ} |$   $-j4 | I_2 | = 0$   $6+j4 | I_3 | 0$ 2-j4 j4 **)**4 4  $\Delta = 2 - j4 \left[4(6+j4) - (-j4 \times -j4)\right]^{\frac{1}{2}} = -1$ -j4[j4(6+j4)-(0x-j4)]+0

100 Lo = 100 + jo

=  $|2 - j\psi|$  100 + jo

= |3 + |0| - |4|=  $|2 - j\psi|$  0 | |4 + |0| | |4 + |4| | |4 + |4| | |4 + |4| | |4 + |4| | |4 + |4| |

T-14 Les 14.245 (-32.9) = - 100 (124 - 16) = - 12400 + 1600 = 0I2 248.39 7-14.93 I2= 0I2 = 2884 44 (-56.3) Iraw loop custent based on = 11.61 (-56.31 - (-14.93) SEP 3: 161.245 (-82.9° V alone 161.245 (-82.9°V 7 short circuit 100 20°V 122 = 2884.44 <-56.31 ILD = 11.61 (-41.38 A I2A = 8.711-j7.67 A By Gramer's Rule

161.245 0 = 2-j4 [4(6+j4) - (-j4×-j4)] = 240 - j64 = 248.39 (-14.93 current theo' 422.  $|\mathcal{Z}| = |\mathcal{V}| \in$ 161.245 (-82.90 = 19.93-1160 6tjy | [I3 Iz 161.245 6tjy (-82.9 (三)4 サブサナンサ (こ)4 12 = 2 jy 0 4(-) 12 jy (-)y

= j159.44 + 1280 + 318.88-j2560 DE2=2-j4 [- (-)4 x(19.93-j160)] = 2-j4 [-(-j79.72 - 640)] = 11.612 (-56.33 - (-14.73) 72 - 022 - 2884, 29 1-56.33 DI2 = 2488 2884.29 (-56.33° 248.39 /-14.93 122= 12-j4 0 122= 12-j4 0 19-93 j160 6+j4 = 2 j 4 (j 79.72 + 640] ISB = 11.612 /-41.4° A IX - 8-71 /-7.68 A I28=8.71-17.68 A By cramer's Rule #2 #4

23 - 12-A - 72-B = (8.711-) 7.67) - (8.71-) 7.68) = 8.711-) 7.67 By Superposition Theo rem

Superposition Theorem De circula 375v2 70V, 0.25v2 Itho 150 R= I1+ I2 Son 250 250 Circuit

The Tay of the problem given in problem step! : Draw loop currents in original current circuits As per superposition theorem, use single power supply (source) at a only DOV source Jish Zin = 120V / I2A 75: Draw loop aucents ISN = IIA - IZA IIA, IZA

Use KVL, find I, A and IZA 20 - 15 |I, A| = |120| -15 - 91.25  $|I_2A| = 0$ IIA = 6.84A I2 A = 1.125 A Step 3 Use only 70 V source Draw loop W 75.25 N 5 N 75.25 N 15 N 70 V Iz B UKE KVL, find IZA, IZB 1502 R = I, B - I2B  $\begin{vmatrix} 20 & -15 \\ -15 & 91.25 \end{vmatrix} = \begin{vmatrix} I, B \\ I2B \end{vmatrix} = \begin{vmatrix} 0 \\ 70 \end{vmatrix}$ = 0.65A, I2B=0.875A I,B According to Superposition theorem, for indesortanding

II = I, A + I, B provided see the direction of I, A and I, B w.r. t II

direction of IIA some as II) =>+ direction of IIB opposite to II) =>

II = + I, A - I, B. = ) petual II = 6.84 - 0.65 = 6.19 A.

I2 = -I2 A+ I2B

direction of I2 opposite to I2A=) (-ve) sign direction of I2 same as I2B -) (+ve) sign.

=-(1.125)+0.875

=-0.245 A (= 0.245 A)

Current in Fir Ras per superposition theorem.

 $T_{7502} = -T_2 A + T_2 B$ = -(1.125) + 0.875= -0.25 A = (0.25 A)

Current in  $5 \times R$  as per superposition Theorem. (4)  $T \times x = I_1 A - I_1 B$  = 6.84 - (0.65) = 6.19 A  $V \times x = I \times x \cdot R$   $= 6.19 \times 5 = 30.95$ 

Using Superposition theorem, we can calculate loop current, current, and thus' each element (R) and voltage awass each element.

Loop arrent in original circuit is equal to the algebric sum of loop arrent when individual voltage source is arting alone.

Therenin Theorem - Ac circuits
Find thereasin's equivalent at termina AB for the circuit shown in figure.
7 (m) 3/4 m
120/45°V
RL=0, No element connected
between ASB.
RTH -> step 1 = ZTH = Effective
RTH -> step 1 = ZTH = Effective Resistance 19 mpedance
Calculate 62 3j42 T-j82 Eurninal From here
6~11j4n
$6xj4 = j24 = \sqrt{0^2 + 24^2} + tan^{-1} \left(\frac{24}{0}\right)$
$6+j4$ $6+j4$ $\sqrt{6^2+4^2}$
$= \frac{24 \cancel{6}}{7.211} \frac{133.69}{233.69} = 3.33 \cancel{6}$

$$= 3.33 \cos(-33.69) + j \quad 3.33 \sin(-33.69)$$
$$= 2.771 - j \cdot 1.85$$

2.771 - j 1.85 series 12 n series j 4 n 2.771 - j 1.85 + 12 + j 4 = 14.771 + j 2.15

Start | 14.771  

$$+j2.15n$$
 |  $-j8n$   
 $(14.771+j2.15)(-j8)$  =  $-j118.168$   
 $14.771+j2.15-j8$  +  $17.2$   
=  $17.2-j118.168$ 

14.771-15.85

To find Voltage a mes - j8vr, we need Iz. 121 1I1 = (V/ 16+14 -j4 | I1 | 120/450 | 12-134+j4 | I2 | 0 | 16+j4 -j4 | I, | = | 120 /45° | 1-j4 | 12 | I2 | 0  $D = \begin{vmatrix} 6+j4 & -j4 \\ -j4 & 12 \end{vmatrix}$  $= (6+j4)(12) - [-j4 \times -j4] + j^{2}b$ =(72+j48)-(-16)=72+j48+16= 56+148 = 1562+482 tan-1 (48)

 $= \frac{73.76}{288 + 148} = \sqrt{88^2 + 48^2} \tan^{-1}(\frac{48}{88})$ 

100.24 /28.61


=4.788 [-73.61° A = IZ = 4.788 cos (-73.61) + j 4788 5)n (-73.61) = 1.35 - j 4.59 A = I2 Vanuss - j8 n = I2 x - j8 = V= IR = IZ = 4.788 L-73.61 x -j8 =(1.35-j4.59)(-j8)  $= -16.8 + j^2 36.72$ VTH = -10.8 -36.72 = -47.52 V. Therenin equivalent circuit. V74 9 274

-47.52 7.51 L-60.13 VZ VTH

The venin's Theorem circuits Find the open circuit voltage at AB, Thevenin's Resistance at AB and cercent this' the resistance AB as shown in figure. Draw Thevenin's equivalent circuit. R13332 = 20V 1. Apply Therenin's Theorem access 2. food doad Resistance RL = Resistor accoss AB = 1/2 3. Calculate Therenis's Resistance RTH 3.1=) Remove RL A Kering 612 A W 512 412 \$3.331 = 20V

A the Son (source by southing) calculate effective (total) resintance standary from opposite side of (to tal resistance) from the thevenin's 3.2, Replace Voltage source by Short circuit, (Replace current 804742 by open circuit) RTH => booking back resintance To the above circuit, find RTH Replace all sources by their internal resistance. terminal AB.

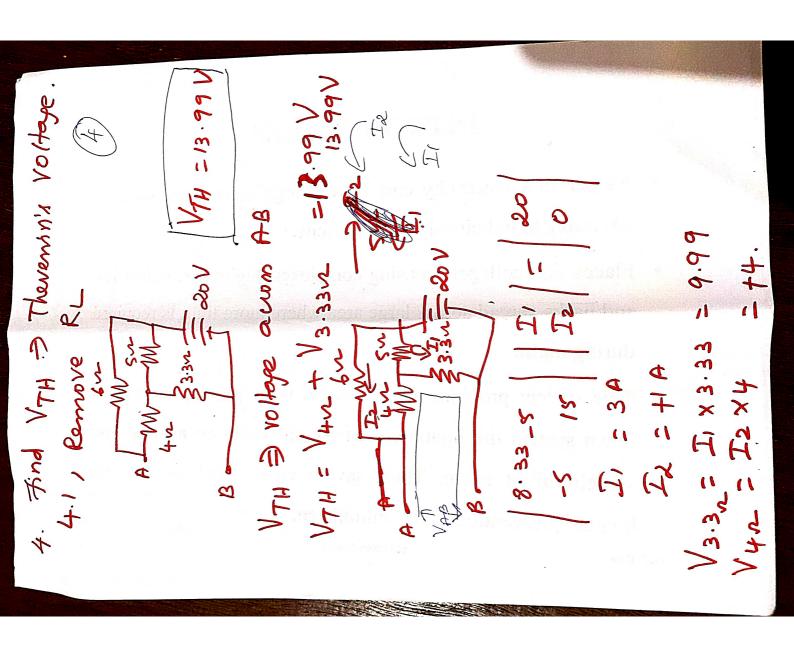45 series with 1.992 12.99 R 62 parallel 5.992 523 3.33 m paralle/ 7 + 1.99 62 5 99 m Sx3.33 = 1.99 RTH= 2.99 m 645.349 66.5×9 5+3.33 8



6. Calculate Load current IL 5. Draw Therenin equival >/~ L - 13.99 ==3.5A IL is faming RL 13.99V BYR R74+ RL cicuit. RTH IL = VTH 2.79 +1

AC transient - Parallel. Find Transient currents i, (t) and i2(t) for the given circuit i, (t) 100 sinsot Ac parallel circuit Two loops =) i, (t) and i2(t) Loop (1) so i, (t) + so(i, (t) -i2(t)) = 100 8in sot soi, (t) + soi, (t) -soiz(t) = 100051050t 100i, 1t) - spiz (t) = 100 sin spt By Laplace Transform 100 IIIs) - 50 I21s) = 100. 50 100 I, 15) - 50 I215) = 5000 52+502

sess - 21+ 80005 = -SD I, 15) + I215) [SD+106] =0 -(2) Loop (12(t) - 1, (t)) + 1 (1, 10-6) (2) (2) (2) 25+20-- 50 b | [] (S) | | Sabo By matein, find I,15), Ix15) 0= (SIT gOI+ (SIT as + (SI') = 0 Soialt) - soi, 1+1+106 Sizit Jet =0 -SDIIS) + Ix(s) (SD + 10 / 2 = 0 50 + 10° I2 15) Ry Leplane Trams from 01+05 05-25425 021(K) = 1 SDD 20 + 10 05- 001/50 001

$$DI_{1}(s) = \frac{550^{2}}{s^{2} + 50^{2}} \left( \frac{505 + 10^{6}}{s^{5}} \right) \left( \frac{5}{s^{5}} \right)$$

$$= \frac{5000}{(s^{2} + 50^{2})} \left( \frac{505 + 10^{6}}{s^{5}} \right) \times \frac{55000 + 10^{6}}{(s^{2} + 50^{2})} \left( \frac{505 + 10^{6}}{s^{5}} \right)$$

$$= \frac{2500005}{(s^{2} + 50^{2})} \left( \frac{505 + 10^{6}}{s^{5}} \right)$$

$$= \frac{255000}{(s^{2} + 50^{2})} \left( \frac{25506}{s^{5} + 10^{6}} \right)$$

$$= \frac{1005}{(s^{2} + 50^{2})} \left( \frac{55006}{s^{5} + 10000} \right)$$

$$= \frac{1005}{s^{5} + 5000000}$$

$$= \frac{1005}{s^{5} + 5000000}$$

$$= \frac{1005}{s^{5} + 5000000}$$

ρ s<sup>2</sup> + 40000 β s + 8 s + 40000 β + cs<sup>2</sup> + 2500 C = 100 S + 2000000 s<sup>2</sup> (β + c) y + s (4000 β + β) + (40000 β + 2500) = 100 S + 2000000 compacing similiar S' terms in LHS with RHS

A+C = 0 40000 A+B = 100 40000 B+2500C = 2000000 By Mathix, find A, B, C

(1

100

$$B = 5^{2} + 5^{2}$$

$$C = -1.249 \times 10^{-3}$$

$$C = -1.249 \times 10^{-3}$$

$$C = -1.249 \times 10^{-3}$$

$$A^{2} + 5^{2}$$

$$A^{$$

$$= \frac{100}{5^2 + 50^2} \cdot \frac{5}{5 + 40000}$$

$$I_{21S}$$
) = 100 8  
 $(S^2 + SD^2)(S + 40000)$ 

By Parkal Faction

$$= \underbrace{A + B}_{2} + \underbrace{C}_{3} = I_{2}(5)$$

52+502 5+40000

cross multiply, Dr cancel

(AS+B) (S+40000) + 
$$((S^2+50^2)=1008$$

AB2+ 40000 AS + BS +40000 B + CS2

40000A +B = 100

40000B + 2500C = 0

By matrix, find A/B, c 40000 1 0 A = 2.499 X10-3 B = 1.562×10-4 -2.499 X15-3 IZIS) = 2.499 X10 3 x + 1.562 X10-4 s2 +502 - 2. 499 XID" 5+40000  $= 2.499 \times 16^{-3} \left( \frac{5}{5^2 + 50^2} \right) + \frac{1.562 \times 16^{-1}}{50} \left( \frac{50}{5^2 + 50^2} \right)$  $2.499 \times 16^{-3} \left( \frac{1}{5+40000} \right)$ By Inverse Laplace Transform. i2(t) = 2.499×163 cossot + 3.124×10 sinsot -2.499×10-3 e -40000t A

Ac Transient Response RL series circuit Find teamient current for the given circuit when switch is closed at t=0in TO Silt) 35H AC RL series circuit 50 sin 25t (Ac power supply) By XVL, write differential equation Rilt) +L dilt1 = V 10 i(t) + 5 di(t) = 50 xin 25t By Laplace Transform Sinat = a
827a2 10 IIs) +5 (SIIs) - i10)] = 50.25 10 I(s) + SAI(s) = 1250 I(s) [10+58] = 1250

$$I(s) = \frac{1250}{(s^2 + 25^2)} \underbrace{(5s + 10)}_{(s^2 + 25^2)} = \frac{250}{(s^2 + 25^2)(s + 2)}$$

$$= \frac{1250}{(s^2 + 25^2)} = \frac{250}{(s^2 + 25^2)(s + 2)}$$
By Portial Faction.
$$(s^2 + a^2) = (s + ja)(s - ja)$$

$$(s^2 + a^2) = (s + j25)(s - j25)$$

$$(s^2 + 25^2) = (s + j25)(s - j25)$$

$$I(s) = \frac{250}{(s + j25)(s - j25)(s + 2)}$$

$$= \frac{A}{(s + j25)} + \frac{A}{(s - j25)(s + 2)} + \frac{C}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s - j25)(s + 2)} + \frac{B}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{B}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{B}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{B}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{B}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{B}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{B}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{B}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{B}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{B}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{B}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{B}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{B}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{B}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{B}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{B}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{A}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{A}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{A}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{A}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{A}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{A}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{A}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{A}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{A}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{A}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{A}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{A}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{A}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{A}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{A}{(s + j25)(s + 2)}$$

$$= \frac{A}{(s + j25)(s + 2)} + \frac{A}{(s + j25)(s + 2)}$$

$$((2+j25)(-2-j^27)=250$$

$$\frac{4+j50-j50-j^2625}{(4+j50-j50-j^2625)}=250$$

$$((4+625)=250$$

$$629C=250$$

$$C=\frac{250}{629}=0.3975$$

$$B(5+j25)(5+2)=250$$

$$B(5+j25)(5+2)=250$$

$$B[j25+j25)(j25+2)]=250$$

$$B[j^21250+j100]=250$$

$$B[-1250+j100]=250$$

$$B=\frac{250}{-1250+j100}$$

A put s= -j25 A(5-j25)(5+2)=250A (-j25-j25) (-j25+2) = 250 A(-j50)(-j25t)=200A (j<sup>2</sup>1250-j100) = 250 A (-1250-)100) = 250 A = 250 -1250-1100. Co. eff of A and B is imaginary
so do partial fraction in a
different method.

$$I(s) = \frac{250}{(s^2+2s^2)(s+2)}$$
we have  $x^2+a^2$  in Denominator
write as  $\frac{As+B}{s^2+a^2}$ 

$$I(s) = \frac{As+B}{s^2+a^2} + \frac{C}{(s+2)} = \frac{250}{(s^2+2s^2)(s+2)}$$
(By Parkial Frontian)
cross multiply
$$(As+B)(s+2) + ((s^2+2s^2) = 250$$
Common Dr get cancelled out
$$As^2+2As+Bs+2B+(s^2+C2s^2=250)$$
Group like terms of s

 $S^2[A+C] + S[2A+B] + [2B+625C]$ Comparing S co.eff in RHS and LHS

$$A + C = 0$$
  
 $2A + B = 0$ 

of A, B, C

co eff of A,B,C is a real number and not i mayinary number.

$$T(s) = \frac{-0.48 + 0.79}{8^2 + 25^2} + \frac{0.4}{5 + 2}$$

$$= \frac{-0.48}{8^2 + 25^2} + \frac{0.79}{8^2 + 25^2} + \frac{0.4}{5 + 2}$$

By 9merne deplace Transform ilt).  $\frac{s}{s^2 + a^2} = \cos at$ a = sinat x2+a2 \_\_ = e - at  $T(s) = -0.48 + 25 \left( 0.79 \right) + 0.4$ Arranging to apply formula  $= -0.4/3 + 0.79 / 25 + 0.4/1 / 8^2 + 25^2 + 0.4/1 / 8+2$ i(+)= -0.4 cos25t + 0.0316 xin25t +0.4e-2t A.

DC Transient Response from a

DC circuit

DC power supply

Whole numbers for power

Eupply eg. 10, 20, 30....

AC Transient Response

AC circuit

Ac circuit

Ac power supply

Number along angle or some

teignometric functions.

eg. 10 Lo°V

25 L63°V

100 sin wt, 1000 sin sout

15e

AC-Tramsient-RLC series circult Determine Transent current opn for the T given circuit: 100 150 sin 200t - Ac power supply AC RLC series d'reuit. By KVL, differential equation 10 i(t) + D.5 di(t) + 1 \_\_ 6 (i(t) dt 200×15 = 150 sin 200t By Laplace Transform 10 IIs) + 0.5 [8](s) - (10) ] + 5000, Is) = 150.200 52+2002 10 IIs) + 0.5 s IIs) + 5000 IIs) I(s)  $[10+0.55+5000] = \frac{30000}{5^2+200^2}$ IIS) [10x+0.5x2+5000]

0.5A+C = 0

10A+0.5B+D=0

5000A+10B+40000C=30000

5000B+40000D=0

By matrix find value of

A, B, C, D.

Subotite in IIs), simplify it.

By governe Leplace Tromsform

find i(t).

Damping conditions Natural frequency wn = 1 rad/sec Damping ratio S = R (no unit)

2 \( \frac{1}{LC} \)

damped frequency \( \omega\_d = \frac{1}{LC} - \left( \frac{R}{2L} \right)^2 \)

rad | sec
\( \omega\_d = \omega\_m \sqrt{1-\delta^2} \)
rad | sec Over damped (R)27/1c  $\left(\frac{R}{2L}\right)^2 = \frac{1}{LC}$ 

Oscillatory in nature  $\left(\frac{R}{2L}\right)^2 \leq \frac{1}{LC}$ =) critical damping =) over damping 0 2 1 5 >1 =) under damping Natural Response / Free Response when a circuit containing storage elements which are independent of sources, the response depends upon the nature of the circuit and is called as vatural Response or free Response torced Response When a source acting on a circuit, the response depends on the nature of such source (external). The behaviour is determined by the application of external energy is called as forced response.

Frank And Architecture (7 loupled circuits Self induced emf, e Earl induced in the coil due to change in its own flux linking with it. self inductance, L It is the property of a coil by which it opposes the change in the value of weeent or flux theory h it due to production of self induced emp Untrally induced emf The emf induced from the coil due to the change in the flux linking, it I the flux being produced by the current in another wil. Neutral Inductance (M) The ability of the first coil to produce an emf in the second coil placed near it, due to change of mount or flux in the first coil. Coupled circuit another through mutual induction, then the two aucuit ale said to lu coupled. Dot Rule for coupled circuit If the accents in two mutually coupled with enter the dotted and or leaves the dotted ends, Mterms will have the same sign as I terms.

If the cureent in one coil enters the dotted end and is the other the cureent leaves the dotted end, Mterms well have the opposite sign as I term. Co. efficient of coupling It is defined as the fraction of the magnetic flux produced by the current in one coil that link the other coil: Self induced conf,  $e = Nd\phi = L di$ Self inductance,  $Z = N\phi$ Co. eff of coupling K = M/VL,L2 Xm = K VX1X2. K = \$12 (faut II) \$1 flux of Iwil) Two coupled coils with self inductances &, and 22

Two coupled coils with self inductances of and a and multiple inductance M have 100 turns and soo turns respectively. A culeent of (A is passed through coil I due to which a flux of is set up. The portion of the take with with coil I alone is I multiple and that link both will land 2 is 0.3 mwb find Li, L2, M and K.

Total flux 
$$\phi_1 = \phi_{11} + \phi_{12}$$
 $= 1 \times 10^{-3} + 0.3 \times 10^{-2} = 1.3 \times 10^{-3} \text{ wh} = 1.3 \text{ mwh}.$ 
 $H = \frac{N_1 \phi_1}{\lambda_1} = \frac{100 \times 1.3 \times 10^{-3}}{1} = 0.13H$ 
 $M = \frac{N_2 \phi_{12}}{\lambda_1} = \frac{580 \times 0.3 \times 10^{-3}}{1} = 0.15H$ 
 $K = \frac{\phi_{12}}{\phi_1} = \frac{0.3 \times 10^{-3}}{1.3 \times 10^{-3}} = 0.23$ 
 $\psi_1 = \frac{M}{1.3 \times 10^{-3}} = 0.23$ 
 $VL_1 L_2 = \frac{M}{K} = \frac{0.15}{0.231} = 0.65H$ 
 $L_2 = \frac{0.65^2}{0.13} = 3.25H.$ 

Two coupled with self indutances Li and L have soo tarns and 1000 turns sispertively. The co. eff of coupling between them is 0.8. The portion of flux that links both the coils when a current of 5A flows through will in 0.9 cob. Find values of Li and L2.

Self inductance of coil 1, 
$$\lambda_1 = \frac{N_1 \phi_1}{i_1}$$

$$K = \frac{\phi_{12}}{\psi_1} \Rightarrow \phi_1 = \frac{\phi_{12}}{K} = \frac{0.9}{0.8} = 1.125wb$$

$$\lambda_{1} = \frac{560 \times 1.125}{5} = 112.5 H$$

$$M = \frac{N_{2} \psi_{12}}{i} = \frac{1060 \times 0.9}{5} = 180 H$$

$$\lambda_{1} = \frac{560 \times 1.125}{5} = 112.5 H$$

$$\lambda_{1} = \frac{N_{2} \psi_{12}}{i} = \frac{1060 \times 0.9}{5} = 180 H$$

$$\lambda_{1} = \frac{1060 \times 0.9}{5} = 180 H$$

$$\lambda_{1} = \frac{1060 \times 0.9}{5} = 180 H$$

Two coupled with self inductances L1 = 0.04 H and L2 = 0.16H and co. eff of coupling K=0.6 has 800 turns in coil 2. The current in coil 1 is 1,= 10 sin soot. Find the voltage induced in coil 2 and maximum qua set up by coil 1. 4 = 0.04H, 62= 0.16H, K=0.6, N2=800 j' = 10 8iu 200f.

M = K VLIL2 = 0.6 Voiot x0.16 = 0.048H

 $e_2 = M \frac{di_1}{dt} = 0.048 \frac{d}{dt} (108in 500t) = 240 cos 500t$   $e_2 = N_2 \frac{d}{dt} = 0.048 \frac{d}{dt} = 0$ 

= 6 × 10 -4 sin soot wb

\$\\ \frac{\psi\_1 = \psi\_{12}}{\times 6 \times 10^{-4} \times \in 500 t} = 10<sup>-3</sup> sin soot wb.

\$1 = 10-3 wb = 1 mwb.

Two coupled costs have self inductances  $L_1 = 2H$ ,  $L_2 = 6H$ . The co. eff of coupling between other is 0.5. It a cuescos  $i_1 = 4 \sin (40t - 30^\circ) A$  flows through coil 1 and  $i_2 = 2 \sin (40t - 30^\circ) A$  flows through coil 2. Find the voltages across coil 1 and coil 2, if the mutually induced conf opposes the self induced emf. H = 2H  $1 L_2 = 6H$  1 K = 0.5 1  $i_1 = 4 \sin (40t - 30^\circ)$   $i_2 = 2 \sin (40t - 30^\circ)$ .

 $M = K \sqrt{4 L_2} = 0.5 \sqrt{2x6} = 1.732 H$   $Voltage agnoss coil 1, V_1 = a L_1 di_1 - M di_2 dt$  = 2 d (4 sin(40t-300)) - 1.732 d (2 sin(40t-300)) dt = 300

= 181.44 cos (40t-30°) V.

Voitage auross voil 2,  $V_2 = L_2 \frac{di_2}{dt} - M \frac{di}{dt}$ 

= 6 d (2 sin (40t-30°)) -1.732d (4sin (40t-30))
dt

= 202.88 cos (40t-30°) V.

Network Functions Ti Jim N/W O/P POXt port Network function: Ratio of response (0/p) to eacitation (2/p) port: A pair of terminals at which an electrical signal enters or leaves a N/w. port => terminals Network Functions: 1. 9 repedance Functions Vi Ti Ti 2. Admittance Functions Ti Vi Vo

Voltage Gain = Vo Vi Gain = 0/p (2) accept Gain = Io Dring Point Functions 1. Driving point impedance Ti To 2. Driving Point Admittance Ii , Io calculated either at i/p port or at olp port only. also called as operational point functions or as operational functions

Transfer Function 1. Transfer / Transform Impedance Vo Ti 2. Tramfer / Transform Ad mi Hance Transform / Transfer Rako 3. Voltage Transfer Ratio

Poles and zeros of a N/w function  $N(s) = \frac{A(s)}{B(s)} = \frac{Nr}{Dr}$  $N(s) = (s+1)^2 (s+5)$ (S+2) (S+3+j2) (S+3-j2) Roots of Nr polynomial => zeros Roots of Dr polynomial =) poles. Zeros: S=-1, S=-1, S=-5 Poles: S=-2, S=-3+j2,5=-3-j2 N(s) = K(s-21)(s-22)....(s-2m)· · · · (s-PN) (S-P1) (S-P2) M > no. of seros N > no. of poles K > scale factor. It N7M, there are (N-M) zeros at infinity

If M7N, there are (M-N) poles at infinity. Using sews and Poles, NIS) represented NIS) = K(5+1)(5+1)(5+5) (5+2) (5+3-j2) (5+3+j2) Stability of a N/w function All poles and sews must lie in Left Hand side of s-plane. S= 5+jw 5 -> real part jw ) imagi navy 5 - plane

Find the deiving Point impedance of the network shown in figure. airen circuit is in t' domain. Transform the given circuit into 't' domam parallel 4+ <u>1</u> 35 All elments in series

$$= 1+2s+\frac{4}{12s+1}$$

$$= \frac{12s+1}{12s+1}$$

$$= \frac{12s+1}{12s+1}$$

$$= \frac{24s^2+14s+5}{12s+1}$$

$$= \frac{21s}{12s+1}$$

$$= \frac{21s}{12s+$$


$$\frac{65}{2+35} + \frac{4}{5}$$

$$\frac{65}{2+35} + \frac{4}{5} \times \frac{58}{205^2+1}$$

$$\frac{68}{2+38} + \frac{48}{205^2+1}$$
Series with  $\frac{65}{2+38} + \frac{45}{205^2+1} + 8$ 

$$\frac{65}{2+38} + \frac{45}{205^2+1} + 8$$
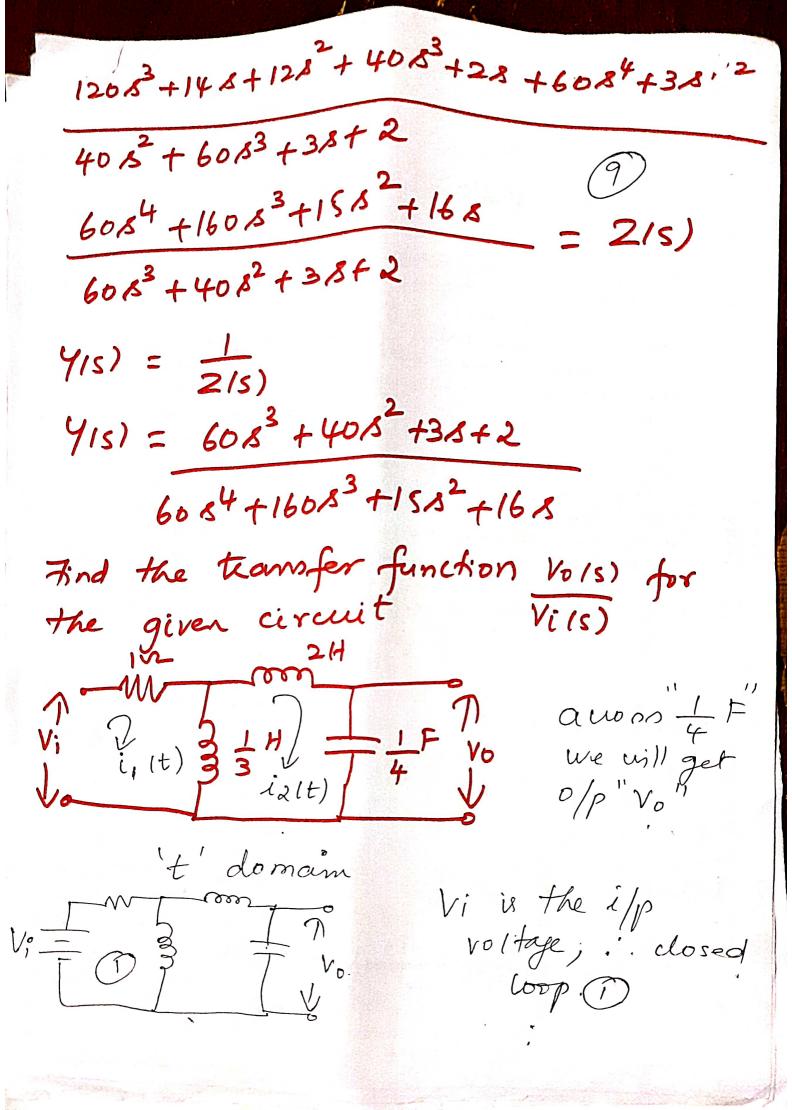
$$= \frac{68(208^2+1) + 48(2+38) + 8(2+38)(2+38)(2+38)}{(2+38)(208^2+1)}$$



Transform the given circuit into 's' domain 25

$$V(1|S)$$
  $V_{1}(1|S)$   $V_{2}(1|S)$   $V_{3}(1|S)$   $V_{4}(1|S)$   $V_{5}(1|S)$   $V_{5}(1|S)$ 

$$D = \frac{3+5}{3} \left[ \frac{7\kappa^2 + 12}{3\kappa^3} \right] - \left[ \frac{-5}{3} \times \frac{-5}{3} \right]$$

$$= \frac{21\kappa^2 + 36 + 7\kappa^3 + 12\kappa}{9\kappa} - \frac{\kappa^2}{9}$$

$$= \frac{189\kappa^2 + 324 + 63\kappa^3 + 109\kappa - 9\kappa^3}{81\kappa}$$

$$= \frac{54\kappa^3 + 189\kappa^2 + 108\kappa + 324}{81\kappa} = \Delta.$$

$$V_0(s) = I_{\kappa}(s) \cdot \left( \frac{4}{3} \right)$$

$$D I_{\kappa}(s) = \left| \frac{3+6}{3} \right| V(s)$$

$$DI_{\lambda}(s) = V(s) \cdot \frac{\Delta}{\Delta}$$

$$I_{\lambda}(s) = DI_{\lambda}(s)$$

$$= Vi IS) \cdot A \times 81 A$$

$$= X \cdot 4$$

$$= X$$

In the given circuit find Vils) 工is) Vols) Ii 15) 1,H) (1) 1/3 3 = 3 F Z S N VO in 't' domain aiver circuit 's' alomain 45 Transform to Ii(s) T) Vi(s) Zin 325 Tis Zsn Vois) Since mode is given, do modal analysis Nodal analysis => KCL 1 48 1 5 45 Vols) 1=+1+1/35 45 46

= 768x3 + 1216x2 + 320x + 432 - 80 = 16/60x2+20x+15+48x3+16x2+12) - 80 D=1122+48+3 = 60x2+20x+15+48x3+16x2+12 - 1 D4 E+B++ 201 F ١, 至1-T; 15) 0 しかのゆんし 128082 28082 2000 5+48 チー 200 (s, 1, 4 (s/ex (2115) 0

Vils) = 5+48 (128022) = 76883 +12168 + 3208 + 352 Vis) = 0 Vis) = Iis) . S+48 x 12802 DY:15) = (I:15) = 5+46 . Jils) - 0 1280 62 76863+121662+352+352... a 2+48 200

- 320 + 256 d - 320 + 256 d

1 3. えムナナ

9.663+15.202+48+4.4

Jiis) 200 (76823 H2165+3208+352)

$$D \ Vo(s) = \frac{12x^{2} + 4x^{43}}{4x} \qquad T(is)$$

$$= -\frac{1}{4x} \qquad D$$

$$= -\left(\frac{1}{4x} \qquad T(is)\right) = \frac{T(is)}{4x}$$

$$Vo(s) = \frac{D Vo(s)}{D}$$

$$= \frac{T(is)}{4x} \times \frac{1280x^{2}}{768x^{3} + 1216x^{2} + 320x + 352}$$

$$\frac{Vo(s)}{T(is)} = \frac{1280x^{2}}{4x} \left(\frac{768x^{3} + 1216x^{2} + 320x + 352}{4x}\right)$$

$$= \frac{320x}{768x^{3} + 1216x^{2} + 320x + 352}$$

$$= \frac{320x}{768x^{3} + 1216x^{2} + 320x + 352}$$

 $=\frac{48}{9.68^3+15.28^2+48+4.4}$ 

Find the poles and the given Network. NIS) = 2 st) and poles are at 4 | s²+5 s+6) and poles are at infinity?

Draw Pole - zero plot / graph . check the stasility of the given N/w function. N/s) = 2 8+1 4(82+58+6) = 2 (1/2) 4 ( 52+58+6)  $K = \frac{2}{4} = 0.5$ zeros =) Roots of Nr. 28+1 =) 28=-1= 0.5 Poles =) Rooth of Dr  $4(x^2+5x+6)=0$ . s=-2, s=-3 No. of zeros = M = 1 No. 08 poles = N=2

Zeros at infinity = N-M= 2-1=1 poles at infinity = M-N= 1-2=(-1) If NOM, sews at intinity Not applicate pole - zero plot "is drawn in s-plane X X 0 5 -jw X-axis =) of = real part of root Y-axis =) jw = imaginary part of root

Nork zero ors "O" in graph

Mark poles as "x" in graph

If all poles and seros lie on the left Hand side (LHS) of s-plane, 3 the network function is stable. The given function is stable. Find the driving point impedance across
AB for the given circuit. Draw
pole - zero graph. Check the stability of the system. 315 A 1H 332 2F 1 34H B T 26 s-domain 't' domain 215) = (3+45) //  $(15+\frac{1}{28})$  series 215) = (3+48) (8+ 1) RIR2 RITRA (3+45)+(3+1)

$$= \frac{8s^{3} + 6s^{2} + 4s + 3}{10s^{2} + 6s + 1} = 2/s$$

$$= \frac{Nr}{10s^{2} + 6s + 1}$$

$$= \frac{Nr}{21s} = \frac{Nr}{2} = \frac{Nr}{2}$$

.. No. of poles at continity = M-N Pole- 200 graph -jw s- plane All poles and seus lie in LHS of : The given Network function/system is stable. s-plane.

Module - 3 Transform a circuit in 't' domain Into a circuit in s' domain and vice versa circuit comists of power supply (energy source) and elements (R, L, C) vice versa circuit comists Resistor (R) 12 Vt = It Rt t > t domain VR(t) = Voltage accors Resistor in to domain  $V_R(t) = I_R(t).R_t$ IR(t) = VR(t) Rt VRIS) = voltage avoss VRIS) = IRIS). RS Resistor in 's' do main Rt = Rs = RVRIS) = IRIS) R L = 6 R Conductance IRIS) = VRIS)

= GKVRIS)

Impedance = 
$$\frac{V}{I}$$
 =  $\frac{V}{I}$  =  $\frac{V}$ 

Transform Equation VL (s) = L [S I(s) - i(10)] = LSILIS) - Lillo) V\_15) + Li2(0) = Lx I2(5) Virs) = L&IL(s) Transform Impedance ZL15) = V115) = LS IL15) = LS ILIS) ILIS) La value of the inductor.  $T_{L}(s) = \frac{1}{L} \int \frac{V_{L}(s)}{s} + \int V_{L}(t) dt$ (VLIt) at = Lillot)  $T_{L(S)} = \frac{1}{L} \left[ \frac{V_{L(S)}}{S} + \frac{L_{IL(O+)}}{S} \right]$ NLIS) + 1/10+) = I/(s)

$$= \frac{V_{L}(s)}{Ls} = I_{L}(s) - \frac{i_{L}(o^{+})}{s}$$

$$= \frac{V_{L}(s)}{Ls} = I_{L}(s) - \frac{i_{L}(o^{+})}{s}$$

$$= \frac{V_{L}(s)}{Ls} - \frac{i_{L}(o^{+})}{s} = I_{L}(s)$$

$$= \frac{V_{L}(s)}{Ls} = I_{L}(s)$$

$$= \frac{I_{L}(s)}{Ls} = \frac{I_{L}(s)}{Ls} = \frac{I_{L}(s)}{Ls}$$

$$= \frac{I_{L}(s)}{V_{L}(s)} = \frac{I_{L}(s)}{V_{L}(s)} = \frac{I_{L}(s)}{Ls}$$

$$= \frac{I_{L}(s)}{V_{L}(s)} = \frac{I_{L}(s)}{V_{L}(s)} = \frac{I_{L}(s)}{V_{L}(s)}$$

$$= \frac{I_{L}(s)}{V_{L}(s)} = \frac{I_{L}(s)}{V_{L}(s)} = \frac{I_{L}(s)}{V_{L}(s)} = \frac{I_{L}(s)}{V_{L}(s)}$$

$$= \frac{I_{L}(s)}{V_{L}(s)} = \frac{I_{L}(s)}{V_{L}(s)} = \frac{I_{L}(s)}{I_{L}(s)}$$

$$= \frac{I_{L}(s)}{V_{L}(s)} = \frac{I_{L}(s)}{V_{L}(s)} = \frac{I_{L}(s)}{I_{L}(s)}$$

$$= \frac{I_{L}(s)}{V_{L}(s)} = \frac{I_{L}(s)}{V_{L}(s)} = \frac{I_{L}(s)}{I_{L}(s)} = \frac{I_{L}(s)}{V_{L}(s)}$$

$$= \frac{I_{L}(s)}{V_{L}(s)} = \frac{I_{L}(s)}{I_{L}(s)} = \frac{I_{L}(s)}{I_{L}(s)} = \frac{I_{L}(s)}{I_{L}(s)}$$

$$= \frac{I_{L}(s)}{I_{L}(s)} = \frac{I_{L}(s)}{I_{L}$$

Transform Equation

$$V_{c}(s) = \frac{1}{C} \left( \frac{T_{c}(s)}{s} + \frac{2(0+)}{s} \right)^{\frac{1}{2}}$$

$$\frac{2(0+)}{s} = \frac{1}{C} \left( \frac{T_{c}(s)}{s} + \frac{1}{2(0+)} \right)^{\frac{1}{2}}$$

$$= \frac{1}{C} \left( \frac{T_{c}(s)}{s} + \frac{1}{2(0+)} \right)^{\frac{1}{2}}$$

$$= \frac{T_{c}(s)}{Cs} + \frac{V_{c}(0+)}{s} + \frac{V_{c}(0+)}{s}$$

$$\frac{T_{c}(s)}{Cs} = \frac{V_{c}(s) - V_{c}(0+)}{s}$$

$$\frac{T_{c}(s)}{cs} = \frac{V_{c}(s) - V_{c}(0+)}{s}$$

$$\frac{T_{c}(s)}{cs} = \frac{V_{c}(s)}{s} = \frac{1}{Cs}$$

$$\frac{T_{c}(s)}{T_{c}(s)} = \frac{1}{Cs}$$

Vc (0+) Ic (+) Iccs) VC10+) Vc(s) 's' domain Ic(s) = C(S Vccs) - Vcco+)] = cs Vc(s) - c Vc(o+) = Ic(s) Cs Vccs) = Iccs) + C Vcco+) Ic(s)+ CVc(o+) = I/s) Cs VCCs) = IIIs) Transform Admittance 4c (S) = I(S) = CS Ve 15)

In the cht given, Switch S is moved from position is time time time of at 3 time t=0. At time t=0, the werent theo' Inductor capacitor and the Voltage accord capacitor is Vo. And the transform cureent IIs) V = 1 2 (00) V, (H) 2 1, (H) C T - Vo 't' olomain when s is moved from position I and to position 2, Second loop of the circuit is closed (closed loop) Circuit is a series circuit. .. we have to find Transfer Impedance. Civen circuit is in 't' domain To find Transfer Impedame, convert circuit in 't' domain into circuit in 's' domain

V,15) 2 I,(5) circuit in 's' domain Calculate Transfer Impedance using this circuit in 's' domain Transfer Impedance 215) = V15) VIS) = algebric potential drop in the circuit  $V(s) = V_1(s) + LIO - \frac{VO}{2}$ comider the leasing terminal of I,18) 215)= R+LS+L 215) = Sum of all impedantes connected (R, L, C) in series (R, L, c) = V115) + L Io - Vo/s IIIs) = VIS) R+ LS + 1/05

The given network is a perallel (10) combination of the connected (10) inductor L is Io and the vollage connected to the parallel RLC circuit amoss a current source I. At And the transform voltage Vis). time t =0, the amount this accoso capacitor Cia Vo. At time t=0+, the current source I, (t) is

.. we have to find Transform Admittance T 9 61, (+) 8 2 5 120 + To find Transform Admittance, we need circuit in 's' domain Civen irmit is a parallel RLC irmit し そ リト 't' domain

IIIS) (1) 3/2 3/25 (2) To T CS (G) circuit in 's' domain Transform Admittance 415) = I15) = I (s) 415) = + + + + CS = G + L + CS YIS) is the Sum of all impedances connected in parallel because arrow is downward. parallel

[because acrow is downward.

I(s) = I(1) - Io + C Vo IIs) = sum af all cureet sources in circuit. = I115) - Io/s + CVO V(s) = I(s)G+ 15 + 65

porallel element Series R 15 obtain the transform impedance shown in figure. the network shown = 112 = 1 = start calculating

The impedance Starting N/W IF and 4 r are parallel 卡二十二十 USES (5+4) parallel -> 0/p > Transform admittance 

2F and (s+4) are in series (13)  $2F \Rightarrow \frac{1}{3} = \frac{1}{25}$ (S+4) is Transform admittance. In series we need Transform impedance. So cowart Transform admittance into Transform impedance. 5+4 = 1 = 215 (415) = 1 = 215 (215) = 415 (415) = 5+4 = 1 Transform impedance 1 series with 1 25. Sty  $\frac{1}{25} + \frac{1}{5+4} = \frac{(5+4)+25}{25(5+4)}$ 282+88 35+4 282+88 Transform impédance 215)

$$\frac{1}{2}$$
 11  $\frac{28^2+85}{38+4}$ 

$$= \frac{28^2 + 88}{68 + 8}$$

 $= \frac{128^{3} + 648^{2} + 648}{48^{2} + 198 + 4} = \frac{48^{2} + 198 + 4}{128^{3} + 648^{2} + 648} = \frac{415}{128^{3} + 648^{2} + 648} = \frac{415}{128^{3} + 648^{2} + 648}$   $= \frac{48^{2} + 198 + 4}{128^{3} + 648^{2} + 648}$ 

## Module 4

Resonance Resonant forequency fo,  $f_{x} = 1$  Hertz (H2) At resonance  $XL \propto f$  XL = Xc, Z=R  $Xc \propto f$ Hertz (H2) X L = 9 reductive reactance = 271 f L L) value of inductor in Henry for frequency of supply = 50H2. X c = 9 rdustre capacitame = \_\_\_\_ C -> value of capacitor in Farad Impedance Z = R+jX ~ X = net reactance of the circuit X= XL-XC Voltage awass Inductor VL = IXL Voltage aucons Capacitor  $V_c = IX_c$ Voltage aucons Resistor  $V_R = IR$ 

avent in a resonant circuit  $T = \frac{V}{R}$ Quality factor of a coil Q = Resonant frequency Band width Band width BW= (f2-f,) H2 Q= = = XL For the given determine the value of Capacitive resitance and impedance of the circuit.

Words-jxc

Worth  $X_{c} = \frac{1}{2\pi f_{c}} = \frac{1}{2 \times 3.14 \times 50 \times c}$ At Resonance XL = XC XL= 277 = 2 x 3.14 x 50 x 125

XL=7850 =2X3.14X50X25

$$XL = XC = 7850$$
  
 $XC = 7850 = 1$   
 $2\pi fC$   
 $2\pi fC = 7850$   
 $C = 1$   
 $7850 \times 2 \times 3.14 \times 50$   
 $= 1$   
 $= 1$   
 $= 1$   
 $= 1$   

Determine the resonant freq for the circuit 100 0.5mH 10MF W 0002/17 2×3.14 \(\int\_0.5\times\_{16}^3\times\_{10\times\_{10}}^6\) 22.25 KH2. Determine impedance at resonant free, 10H2 above resonant free, 10H2 below resonant forg.

10H2 jon 0.1H 10MF

WOOD + CO

Resonant foreg fr= 1 271 VLC 2×3.14 JO.1 X10 X10- 6 = 159.2H2. 10 H2 above reconant freq 159.2+10 = 169.2 H2. 10 Hz below reconant free 159.2 -10 = 149.2H2. At resonance frequency (159.2 H2) Z= R = 10 n Impedance at 169.2 Hz. 2= R+j X 2 X=XL-XC calculate XL and XC at 169.XH2. XL = 271 L = 2×3.14×169.2× 0.1 = 106.262 XC = 1 = 1 27fC = 2x3.14x169.2x10x16 = +<del>06.2674</del>. 94.11

X= X L-XC= 106.26-94.11 = 12.15 2 = R+jxn = = + j12.152. Impedance at 169.21+2. Impedance at 149.2H2. 2= R+1 X~ X= XL - XC XL= 2HfL = 2×3.14×149.2×0.1 = 93.6988 m  $x c = \frac{1}{2\pi f c} = \frac{2 \times 3.14 \times 149.2}{2 \times 10.01 \times 16}$ X 10×15 6 = 106.731 m X = XL - XC = -13.032 2= 10-13.032 j 2

44 ps

A series circuit with R=1012, L. = 0.1H, C = 50 MF has am (7) applied voltage V= 50 Lo with a Variable frequency. Find the resonant frez, the value of frez at which maximum voltage occurs auss the industry and the value of frequency and the max voltage occurs at which max voltage occurs across the capacitor. fr = 1 = 1 271 VLC = 2×3.14 VO.1×50×156 =71.18H2 fee at which max voltage appear amoss Industry  $\begin{aligned}
f_1 &= 1 \\
2\pi \sqrt{LC} &= R^2C \\
&= 72.08H2
\end{aligned}$ 

free at which mak vo Hage appear across capacitor. (8)  $f_{c} = \frac{1}{2\pi} / \frac{1}{Lc} - \frac{R^{2}}{2L}$ = 71.08 H2. Max. Voltage appear a word Inductor above resonant freq. Max. voltage appear auons capacitor below resonant freg. Determine Bushity factor(Q) of a coil for the series circuit comisting 08 R=101, L=0.1H, C=10MF. Q = Resonant frequency Band width (no frequency, Bandwidth = f2-f1 details provided)  $BW = \frac{R}{2\pi L} = \frac{10}{2\times 3.14\times 0.1}$ = 15.91 Hz

Resonant freg fr = 1 2TT LC = 159.2 Hz 2×3.14×0.1×10×15 = 10 (no unit) Q= 159.2 Determine the value of Q at sesonance and bandwidth of the given circuit. AC Series circuit. \$ 10m (x) 3 5H Q = fr BW 2×3.14 \ 5×100×156 = 7.12 H2.

$$BW = \frac{R}{2\pi L} = \frac{90 + 10}{2 \times 3.14 \times 5}$$

$$= 3.185 H2$$

$$8 = 7.12 = 2.235 (no unit)$$

$$3.185$$
Parallel Resonance
$$Rc \times C$$

$$W = \frac{10}{10}$$

Find resonant fore in ideal parallel LC circuit: 10V Somt 3 TO.01MF  $f_{v} = \frac{1}{2\pi\sqrt{Lc}} = \frac{2\pi\sqrt{50\times10^{-3}\times0.01}}{2\pi\sqrt{Lc}} = \frac{2\pi\sqrt{50\times10^{-3}\times0.01}}{7117.6H2} = \frac{1}{7117.6H2}$ For tank circuit, find resonant 1 - R 2 - R frequency.

1000 000

1000 F

1000 F

1000 F  $= \frac{1}{2\pi} \sqrt{\frac{1}{0.1 \times 16^6}} - \frac{10}{0.1}$ R connected with Lis RL: 106-102 2x3.14 = 158.35H2.

Impedance Vs Frequency " D 4 1 2=R At Resonance 2= R y increases with freq y deres es with fee. so = resonant frequency At lower freq , 2 decreases At higher free, 2 increases. Phone angle Vs forguerry pinuseases at lower freq Cost Lag of deveases at higher freq. for for for for.

Vs Resis tome R Q ynfz Bandu

Three phase Networks Circuits Ac circuit Ac power supply De circuit De power supply ON ON AC circuit three phase circuit Single phase 3 p circuit 1 p circuit three phases
R, Y, B. one phase-P-Industry, commercial HIS V AC supply 50 H2 one neutral-N 230VAC supply 50 HZ 440 V Ac supply SOH2 Leavy loads heso loads domestic

3 phases - combination of three phases R, Y, B phases R, Y, B They differ in phase by 120° 120° R phase angle between REYIR120° .. BER K 120° R 4B = 120 + 120° = 240° B & 4 = 120°+120° = 240° Phose Sequence 1. RYB phase sequence - clock wise direction 2. RBY phase sequence. anticlockwise anticlockwise direction.

RYB phase sequence (or) (3)

Negative phase
sequence

120°

120°

Clockwise direction. VRR = ERR = Vm sin wt Vyy = Eyy = Vm sin(wt -120) VBB= EBB

(T) = Vm sin(wt-240°)

T) Timeperiod. = Um sin (wt +120°) Most commonly used phase sequence is RYB phase sequence.

RBY Phase sequence (or) positive phase sequence 20° anticlock wise direction. 1200 VRR = ERR = Vm sinwt VBB = EBB = Vm sin(wt-120°) Vyy= Eyy= Vm sin (ut -240°)

IRR'RI IBB' V IYY (DOD) R, Y, B - Line Terminals N - Neutral - junction R, Y, B phase Line Voltage Voltage between (R, Y, B lines) VRY, VYB, VBR

Line Current Current this' line R, Y, B IR, IY, IB Between R phase & Neutral N Y phase & N Bphone & N Phase voltage Voltage between phase and Neutral VRN, VYN, VBN phase arrent awent flowing phase room IRR, IYY, IBB IRRI, TYY, I BB' Neutral Current IN & accent flowing theo' neutral

## Basic concept

1. polar to Rectampular form.
Rectangular to Polar form.
(a+ib) (rzo)

2. Star to della transformation. Delta to star transformation.

Star Network

Delta Network

RA MCC

RABY ZR AC

RAB = RARB + RBRC + RCRA RC RAC = RARC + RCRB + RBRA

RB

RBC = RBRC + RCRA + RARB

De Ha Network

star Networ

RAB RAC 3 RBC

3 RA MRC MRC B

RABHRAC TRAC

RC= RACRBC

RAB+RBC+

RAC

RB= RAB RBC
RAB+RBC+RAC

Network Della Network RAB - RARB+ RBRC +RCRA NY = 18nRBC Delta Network

RA: RABRAC RABHRBEFRAC RB = RAB RBC Rc = RAC RBC = 3n Balamed system all R and 2 have same values Un balanced system R and 2 have different values.

No neutral (N) wice A symmetrical 30, 3 wire , 400V supply is connected to a delta connected boad as shown in figure. Impedance in each branch are

2 values are

3 values are

4 values are

5 values are

6 values are

6 values are

7 values are

7 values are

7 values are

8 values are

9 values are

1 values are

2 values are

2 values are

2 values are

2 values are

3 values are

4 values are

4 values are

5 values are

6 values are

6 values are

7 values are

7 values are

8 values are

9 values are

9 values are

1 values are

2 values are

1 values are

2 values are

1 values are

2 values are

2 values are

4 values are

4 values are

5 values are

6 values are

7 values are

8 values are

9 values are

1 values are

1 values are

1 values are

1 values are

2 values are

1 values are

2 values are

2 values are

4 values are

4 values are

5 values are

6 values are

7 values are

8 values are

8 values are

9 values are

9 values are

1 values are

1 values are

1 values are

1 values are

2 values are

2 values are

2 values are

2 values are

4 values are

4 values are

4 values are

5 values are

6 values are

7 values are

8 values are

9 values are

9 values are

9 values are

1 values are

2 values are

1 values are

2 values are

2 values are

2 values are

4 values are 24B = 10 6-45° ~ LBR = 2.5 /60 n Find its equivalent star-connected boad. The phase sequence is RYB. ZBR ZRY
ZYB

9/p voltage = Vm sinut =) for a.c.
arauit

Ac circuit three phase

2 1 po<sup>0</sup> 120° R VR = Vm sinwt Vy = Vm Sin (wt -1200) VB = Vm sin(wt -240°) VR= ER, Em= Vm Line uneant: IL Star connection Ir, Iy, IB. Jer'3 R' IN-Neutral current. Phase current: Iph IRR', Iyy' = IBB! In

Phase Voltage: Vph VRN, VYN, BN Phase R, Y, B and Neutral N-Line Voltage: VL Voltage between lines (R, Y, B) Vo Haye VRY / VYB/ VBR IL = Iph VL= V3 Vph P = V3 YLIL COS P

Della Connection Line luceant: IL IR, IY, IB Phose Curent: Iph IRP', IMY', IBB' phase Voltage: Wph VRY, VYB, VRB. Line Voltage: VL VRY, VYB, VRB

IL= V3 Iph

VL= Vph

P= V3 VLIL cosp

A star connected bad (belanced) of (8+jb) is per phase is connected to a 3\$\psi\$, 230 V supply.

Find Line current, power factor, power, reactive power and to tal volt-Amp star connected boad

IL= Iph P = V3 VLIL cox d VL = V3 Vph Balanced load, all 2 are equal 2 = 8+jbr (all impedance - R, 4, B load and same).

230 V = V\_

VL= V3 Vph

...  $Vph = \frac{V_L}{\sqrt{3}} = \frac{230}{\sqrt{3}} = 132.791 \text{ V}$ = 132.791 \( \frac{1}{20} \text{ V} \)

P= Active Pouver (or) power = V3 VI IL worth W = \( \frac{3}{3} \times 230 \times 13.28 \quad \frac{1-36.87}{} = 4232.30.2-36.87 Watt = 4.232 /-36.87 kilo Watt. Reactive Power (Q) V3 VLIL BIN & VAR - √3 ×230 × 13.28 <u>/-36.87</u> x sin (-36.87°) = 5290.38 <u>\( -36.87 \times - 0.6</u> = - 3174. 228 [-36.87 VAR. Apparent Power (S) V3 YL JL VA = \sqrt{3} x 230 x 13.28 \(\frac{1}{2} - 36.87\) = 5290.38 L-36.87 VA (one phase)

= 3 x Apparent power. = 3× 5290.38 <u>[-36.87.</u> = 15871.14 L-36.87 VA. If needed to collewlate pour in phase use Vph, Iph. If "phase" is specified in problem. A balanced detta, - connected load of (2+j3) or per phase is connected to a balanced 3 \$440 V supply. The phase current is 10A. Find
i) total active power ii) tot Reactive power iii) apparent power. Delta connected board IL = V3 Iph YL = Yph VL= 440 V, Vph= 440 V

$$Z = (2+j3) n$$
  
 $Z = (2+j3) n$   
 $Z = (2+j3) n$ 

To calculate power we need power factor,  $\phi$ power factor cos  $\phi = \frac{Rph}{2ph}$   $\phi = \cos^{-1}(\frac{Rph}{2ph})$ 

7 = (2+j3) 2 = (R+j)

R=2 => Rph

Z = 2+j3 $Y = \sqrt{2^2+3^2} = 3.6$ 

 $\sigma = \tan^{-1}(b/a) = \tan^{-1}(\frac{3}{2}) = 56.31$ 

2 = 3.6 (56.31

 $cos d = \frac{Rph}{2ph} = \frac{2}{3.6} = 0.56$   $\phi = cos^{-1}(0.56) = 55.94$ 

## Active power 1 Total Active Power P = V3 YL IL cos \$ W = 1.732 × 440 × 17.32 ×0.56 = 7391.57 = 7.39157 KW Reactive Power Q = V3 YL IL Sin & VAR = 1.732 ×440 ×17.32 × sin (55.94) = 10934.92 = 16.9349 K VAR Apparent Power (S) = SIVLIL VA 51.732 × 440 × 17.32

= 13199.23 VA = 13.199 KVA

A 3 q, balanced delta - connected (21) bad of (4+j8) r is connected across 400 V, 3 & balanced supply. Determine phase currents and Line currents. Assume RYB phase sequence. Calculates power drawn by the load. VL= Vph , IL = V3 Iph. VL= 400V 2ph = (4+j8) 2 = 8.94 [63.43 Iph = Vph Phase voltages

VRR' = 400 Lo° V = Phase voltage

Vyy' = 400 L-120° V = ... "4" 400 (-240° V = .... "B" VBB =

Phase Cereents IRR' = VRR = 400 20° 2ph 8.94 263.43° = 44.74 (-63.43° A Iyy' = Vyy' = 400 /-120 Zph 8.94 /63.42° = 844.74 <u>1-183.43°</u> A = VBB' = 400 /-240° Zph 8.94 163.43° = 44.74 [-303.43° A. Line currents ILE V3 Iph. IR = V3 IRK' = 1.732 ×44.74 1-63.43° = 77.492-63.43°A IY = V3I44' = 1.732 x44.74 1-183.430 =77.49 [-183.43° A

IB = V3 IBB'=1.732 x 44.74 /-303.43° =77.49 /-303.43° A power drawn by the boad = Active power  $p = \sqrt{3} V_L I_L \cos \phi = Total power.$ VL = 400 V IL = 77.49 \$ = 63.43° 2ph = 8.94 /63.436 P= 1.732 x 400 x 77. 49 x cos 63.43 = 24012.8414 W = 24.013 KW Reactive Power & : V3 VLIL sing VAR. = 48015.31426 VAR = 48.015 K VAR Appenent Power 5= V3 VLIL VA = 53685.072 VA = 53.685 KVA

A balanced star-connected board having an impedance (15+j20) v2 (24) per phase is connected to a 30,440V, 50 H2 Kupply. Find line cereents and power absorbed by the load. RYB phase sequence. IL= Iph VL = V3 Vph  $2 = (15 + j20) = 25 \angle 53.13 \circ 2$ To calculate phase account in each phase, calculate phase in each phase in each phase. VL= 440 V. Vph= VL phase voltage 254.04 Lo° V VRR1 = 4406 = Vyy' = 440 /-120° = 254.04 /-120 V VBB' = 440 /-240° = 254.04 /-240° V

## phase ament

(25)

$$Tyy' = Vyy' = 254104 \angle -120^{\circ}$$

$$= 25 \angle -120^{\circ}$$

$$= 10.16 \angle A = 10.16 \angle -173.13^{\circ}$$

Line current = phase current

Balanced boad = boad in each (26) phase (impedance = Z) are equal Unbalanced boad = boad is different in each phase. For power calculation, calculate power in each phase separately and then add power in three phases to gether. phase current and phase voltage are different for each phase Line voltage and line aucent are different for each phase.

Three impedances 2, = 20 230° n (27) 22= 40 /60° v, 23=10/-90° n (unbalanced load) are cornected to adulta supply of 400% 3 \$ system. Determine phase currents, Line currents, total, power consumed by the load. IL= V3Iph 1 VL= Vph VL= 400 V: phase voltage. V=RR' = 400 20° V Vyy' = 400 4-120°V VBB' = 400 L-240°V 21:2R, 22= Zy, 23 = ZB.

Phase currents

28

IRR = VRR = 400 L0 = 20 L-30° A

Tyy' = Vyy' = 400 (-120° = 10 (-180° A)

Zy 40 (60°

IBB' - VBB' = 400 \( \left( \frac{1}{240} = 40 \left( \frac{150}{10} \right) \)

Line currents

IL = V3 Iph.

IR = \( \begin{aligned} & \text{TRR} & = 1.732 \text{ \text{\chi 20} \int -30°} \\ & = 34.64 \left( -30° \text{ \text{\chi 30°} A} \end{aligned}

IY = \( 3 \times I 44' = 1.732 \times 10 \( L 180' \)
= 17.32 \( \left( -180' \) A

IB = \( \mathbb{G} \times \tim

## Power in R phase = V3 Vph Iph = V3 VRR' IRK' = 13856 L-30°

power in 4 phase = V3 Y44' I44' = 6928 (-300

power in B phase = \( \mathbb{G} \) \( \mathbb{V}\_{\mathbb{B}} \) \( \mathbb{G} \) \( \mathbb{G}\_{\mathbb{B}} \) \( \mathbb{G}\_{\mathbb{B}} \) \( = 277/2 \) \( \alpha \) \( = 396 \)

Total power = Sum of power in R, Y, B phases.

= 13856 +6928+27712 = 48496W

(omit angle part)

## Neutral shift

Neutral point - junction of R14,13 Connect wire to a newtral point

3 Newtral hime (N) Current this' Newtral line is Neutral Current IN IN = - [IR + IY + IB] Newton I shift occurs due to un balanced boad. VN = (VRY X VRN) + (VYB X VYN) + (VBR X VBN)

VRY + VYB + VBR = Sum of product of line voltage and phase voltage Sum of Line voltage.

## Unbalanced Four Wire Star Connected Load Four wire JR, 4, B and Newtral (N) Star - Y Network. Delta - D Network. Newfral point Newfral point owailaste in star Network. Star Network, four wires possible wire means line, R, Y, B, N IN = - [IR + IY + IB]

An unbalanced four - wire, star connected boad has a balanced voltage of 400 V. The boads are Z,=(4+j8) 2 = ZR  $2_{2}=(3+j4)$  = 24 23 = (15 + j20) n = 2Bcalculate line current, current in rental line, total power. VL= 400V IL= Iph VL= V3 Vph. Vph= VL => phase voltage VRR1 = 400 60° Vyy' = 400 /-120 1.732

IL = Iph

IRr' = IR

Iyy' = Iy

IBB' = IB

Newhal Line

Neuhal Line current IN

= - [IR + Iy + IB]

Convert IR, Iy, IB in rectangular form for addition

power in R phase =  $\sqrt{3}$  V\_IIL cos of =  $\sqrt{3}$  V\_RR' IRR' cos of of from 18 in 2R (poler form) R141 B phase connected With Wire - This wire

dine phase V7 Voltage Current Voltage IR  $V_{\mathcal{R}}$ IRRI VRRI Iy Vy I941 Vyy IB VB IBB1 VBB1

Survent flowing this phase Current flowing this IR, IY, IB

18 Network VRN VBN Line Voltage Between Voltage VRY, VYB, VBR phase Voltage Voltage between Neu bal. VRN/ VYN/

Neutsel point Janckion at which, R, 4, B
phase join together. Connecting vive to newball point Wental line
1) Neutral line
1) Current flouring thus
1)
Neutral line is Neutral current. (2N)Only in Star Network, Neutral point, Neutral Current.

Delta Network IB phase aure No renton , IRK', IGY point in deltak IY, IB

Line voltage

Voltage between line

VRY, VYB, VRB.


[NO rentral]

Vphone = Vine

Module 5 Z parometers Impedance = Z = V Impedance paro meters open circuit parameters open circuit impedance parameters. Two port network. Vivi Vi Vi Vi Vi Vi Vi Io Vi Vi Vi Vi Vi Io Vi I For a two port N/w, the i/p and O/p Voltages V, and V2 can be represented/expressed in terms of i/p and o/p arrent I, and Iz. [V] = [Z] [I]

V = RI = IR

 $\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2_1 & 2_{12} \\ 2_{21} & 2_{22} \end{bmatrix} \begin{bmatrix} T_1 \\ T_2 \end{bmatrix}$ VI = Z11 I) + Z12 I2 - 0 V2 = Z21 II + Z22 I2. - (2) From @ and @, find 211, Z12, 221, 222 put  $I_2 = 0$ , open circuit  $I_2$ .  $V_1 = 2\pi I_1$ ZII = VI => % driving point impedance V2= 22/ II Z21 = 1/2 => Forward Transfer II Impedance put I,=0, open circuit I,  $V_1 = Z_{12} I_2$   $V_2 = Z_{22} I_2$ 212 = VI Reverse Transfer Impedame VO/P. driving print Reverse Transfer Impedame VO/P. driving print

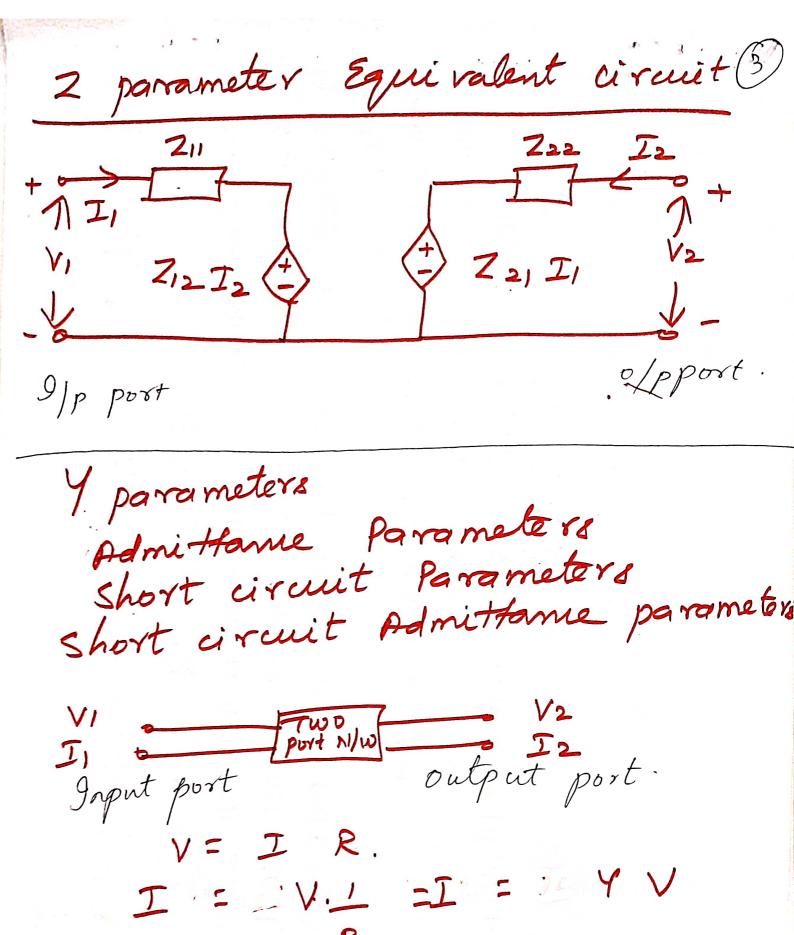

[I] = [Y] [V]

 $\begin{bmatrix}
\overline{I}_{1} \\
\overline{I}_{2}
\end{bmatrix} = \begin{bmatrix}
Y_{11} & Y_{12} \\
Y_{21} & Y_{22}
\end{bmatrix}
\begin{bmatrix}
V_{1} \\
V_{2}
\end{bmatrix}$   $\begin{bmatrix}
\overline{I}_{1} = Y_{11} V_{1} + Y_{12} V_{2} & -1 \\
\overline{I}_{2} = Y_{21} V_{1} + Y_{22} V_{2} & -1 \\
\hline{I_{2} = Y_{21} V_{1} + Y_{22} V_{2} & -1 \\
\hline{I_{3} = Y_{31} V_{1} + Y_{22} V_{2} & -1 \\
\hline{I_{4} = Y_{11} V_{1}}
\end{bmatrix}$   $\begin{bmatrix}
\overline{I}_{1} = Y_{11} V_{1} & Y_{22} & Y_{2} & -1 \\
\hline{I_{1} = Y_{11} V_{1}} & Y_{22} & Y_{2} & -1 \\
\hline{I_{2} = Y_{21} V_{1}} & Y_{22} & -1 \\
\hline{I_{3} = Y_{11} V_{1}} & Y_{22} & -1 \\
\hline{I_{4} = I_{1}} & Y_{23} & -1 \\
\hline{I_{1} = I_{1}} & Y_{23} & -1 \\
\hline{I_{2} = Y_{21} V_{1}}
\end{bmatrix}$ 

put  $V_1 = 0$ , short circuit  $V_1$   $I_1 = Y_{12} V_2$   $Y_{12} = \overline{I_1}$   $V_2$   $Y_{11} = Y_1 = Y_2$   $Y_2 = \overline{I_2}$   $Y_2 = \overline{I_2}$   $Y_2 = \overline{I_2}$   $Y_1 = Y_2 = Y_2$   $Y_1 = Y_2 = Y_2$   $Y_1 = Y_2 = Y_2$   $Y_2 = Y_2 = Y_2$   $Y_1 = Y_2 = Y_2$   $Y_2 = Y_2$   $Y_1 = Y_2$ 

## h parameters Hybrid para meters. Both open and short circuit conditions. V, = h11 I, + h12 /2 -Iz = h2, I, + h22 /2 - 2 write upn for i/p voltage V, and O/p aurent Is. $\begin{bmatrix} V_1 \\ T_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} T_1 \\ V_2 \end{bmatrix}$ Vsing @ and @ find "h" parameters. V2=0, Short circuit V2 I2 = h2/I/

 $V_{1} = h_{11} I_{1}$   $h_{11} = \frac{V_{1}}{I_{1}}$   $h_{21} = \frac{I_{2}}{I_{1}} = \frac{O/P}{I/P} I$   $I_{2} = h_{2}II_{1}$ 

put  $I_1=0$ , open circuit  $I_1$   $V_1 = h_{12} V_2$   $I_2 = h_{22} V_2$   $h_{12} = \frac{V_1}{V_2}$   $h_{22} = \frac{I_2}{V_2}$ 

hii =) input impedame
hai =) forward current gain
hia =) Reverse voltage gain
hiz =) output admittance.

ABCD parameters

Circuit parameters

Circuit parameters

Tranominsion parameters.

Used in power frammission engineering

power frammitted from one end (i/p)

power sending and / port

power seceived at other end (o/p)

receiving and / port

VIJ TWO J+ V2 sending and Receiving end alp port is towards direction of I2 Right side (: receing)  $\begin{bmatrix} V_1 \\ J_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -T_2 \end{bmatrix}$ V, = AV2 -BI2 - $I_1 = CV_2 - DI_2 - O$ uning (1) and (2) find Tparameters. Iz = 0, receiving end is opencircuited I/= CV2 VI = AV2 A = VI C= II

V2

V2

put  $V_2 = 0$ , receiving end is short circuited.  $V_1 = -BI_2$   $I_1 = -DI_2$ 

 $B = -\frac{V_1}{I_2}$   $D = -\frac{I_1}{I_2}$ 

A =) Reverse voltage ratio B => Transfer Impedance

C = Transfer Admittance

D => Reverse Cureent Ratio

Y equivalent circuit

18

Inverse Transmission Parameters.

$$A'B'C'D'$$
 parameters.

 $V_2 = A'V_1 - B'I_1$ 
 $I_2 = C'V_1 - D'I_1$ 

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A & +B \\ C & +D \end{bmatrix} \begin{bmatrix} +V_1 \\ -I_1 \end{bmatrix}$$
 $I_1 = 0$ 
 $V_2 = A'V_1$ 
 $I_2 = C'V_1$ 
 $V_1 = 0$ 
 $V_2 = -B'I_1$ 
 $I_2 = -D'I_1$ 

A' = Inverse Forward voltage Ratio

B' = Inverse teamsfer impedance

c' = Inverse teamsfer admittance

D' = Inverse forward current gain

Paramete r	Condition	s for
	Symmetry	Reciprocity
2	Z11 = Z22	712 = 721
4	411 = 421	Y12 = Y21
h	sh = 1	h12 = - h21
T /	$A = \mathcal{D}$	AD -BC=1
Dh=  hi	, h12 =	(huhaa) - 1626.

 $0h = |h_{11}| h_{12}$  $|h_{21}| h_{22} = (h_{11}h_{22}) - (h_{21}h_{12})$ 

KVL > Z parameters. KCL > Y parameters.

Find 2 parameters for the following Network. Draw equivalent circuit.

 $1+\frac{1}{I}$  21  $1+I_2$   $I_2$   $1+\frac{1}{I}$   $1+\frac{I}$   $1+\frac{I}{I}$   $1+\frac{I}{I}$ 

check the condition for symmetry

and Reciprocity.

from positive of V, , I, flows thus Z, from positive of V2, Iz flows thus' 72 II+ Iz flows thus' 23.

[VI] = [ZI] ZI2 [I]

V2] = Z21 Z22 [I2]

ZII > Sum of impedame in boop 1

= 2/+ 23

$$Z_{22}$$
 = Sum of impedance in loop 2 12  
=  $Z_{21}$  =  $Z_{3}$   
 $Z_{12}$  =  $Z_{21}$  =  $Z_{3}$   
 $Z_{13}$  =  $Z_{21}$  =  $Z_{3}$   
 $Z_{23}$  =  $Z_{21}$  =  $Z_{23}$  =  $Z_{22}$  =  $Z_{22}$  =  $Z_{22}$  =  $Z_{22}$  =  $Z_{23}$  =  $Z_{21}$  =  $Z_{2$ 

$$712 = 221$$
 $23 = 23$ 

The circuit is reciprocal in nature. The following readings are thained 13 experimentally for an em-known two port Networks.

	Vi	Va	II	Iz	
Op open	100V	60V	IDA	D	
i/p open	30V	407	0	3 A	

2 calculate, 2 mben i/p and 0/p
port are open

Open circuit condition = I = 0 Closed circuit condition=V=0

$$\frac{7}{12} = \frac{V_1}{T_2} = \frac{30}{3} = 10 \text{ sz}$$

I2/ Openiercuit 9/p port.

Take V, , I2 when i/p port is open circuited.

= 6 v2 vhen ofpport is open. = 60 Zar= Yr Ofpport open. /Iz=0 222 = V2 I2/II=0 Reci procity Symmetry Z12 7 Z21 211 7 222

An To attenuator is shown in (15) fig. Find the 4 parameters and draw the equivalent 4 parameters to go with the Vi 35kn 32kn V2  $\Rightarrow TT$ Grait wooks like TT (pie) for a TT, it is possible to apply 1= | V) = [I] [ ] = [Y].  $= \frac{1}{1 + \frac{1}{5}} \frac{1}{103} = \frac{1}{103$ 1×10-3 =(1.2×103 = | 4/ 1.5×10 422 421 = 1×163~ Y11 = 1.2 × 10 -3 ~ 422= 1.5×10-3~ 412 = 1×15 3~

711 + Y21 Y12 = Y21 The circuit is reciprocal in nature. On short circuit test, the currents and voltages were determined experimentally for an unknown two port net work.  $I_1 = 1mH$   $I_2 = -0.5mA$ Short circuit  $V_1 = 25V$   $V_2 = 0$   $V_3 = 0$ I, = ImA  $I_1 = 1mA$   $I_2 = -10mA$   $V_2 = 50V$   $V_1 = 0$ . Short circuit  $V_1 = 0$ . 9/p port.  $I_1 = 1 m A$ V2 = 50V Y parameters for short circuit conditions.

Short circuit o/p port

14

$$\frac{y_{11}}{V_1} = \frac{II}{V_1} = \frac{1 \times 16^3}{25} = \frac{40 \, \mu \, v}{700} = \frac{100 \, v}{100} = \frac{100 \, v}{1$$

$$\frac{1}{1} = \frac{1}{1} = \frac{-0.5 \times 16^{3}}{25} = -20 \times 16^{5} \text{ N}$$

short circuit i/p port

$$V_1 = 0$$

$$4/2 = \frac{1}{12} = \frac{1 \times 10^{-3}}{50} = -20 \times 10^{-6}$$

$$422 = \frac{12}{12} = -10 \times 10^{-3} = -200 \times 10^{6} \text{ V}$$

Symmetry

111 # 121 The circuit is

Reciprocal.

