

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

Fifth semester B.Tech degree examinations (S) September 2020

Course Code: EC307**Course Name: POWER ELECTRONICS & INSTRUMENTATION**

Max. Marks: 100

Duration: 3 Hours

PART A*Answer any two full questions, each carries 15 marks.*

Marks

- | | | | |
|---|----|--|-----|
| 1 | a) | Explain the structure of power BJT with neat schematic. | (6) |
| | b) | Explain switching characteristics of power diode with the help of waveform. | (6) |
| | c) | What is the importance of free-wheeling diodes in converters? | (3) |
| 2 | a) | Draw and explain the circuit diagram of Boost converter with inductor current and switching waveform. | (8) |
| | b) | Describe the working of IGBT and draw input and output characteristics. How does latch up occurs in IGBT? | (7) |
| 3 | a) | Define the working of fly back converter with neat diagram. | (5) |
| | b) | Draw the VI characteristics of GTO and list its various modes. | (3) |
| | c) | Explain the working of full bridge isolated converters with help of circuit diagram and relevant waveform. | (7) |

PART B*Answer any two full questions, each carries 15 marks.*

- | | | | |
|---|----|--|------|
| 4 | a) | List any five differences between offline UPS and online UPS. | (5) |
| | b) | With neat circuit diagram and switching waveform explain the working of push pull inverters. | (10) |
| 5 | a) | Explain how to measure an unknown resistance using Wheatstone's bridge with the help of schematic. | (5) |
| | b) | Describe phase vector modulation of three phase inverter. | (5) |
| | c) | Define the following Static Characteristics:
i) Accuracy ii) Precision iii) Repeatability iv) Reproducibility v) Resolution | (5) |
| 6 | a) | List any two differences between half bridge and full bridge inverter. | (3) |
| | b) | Explain different classification of instruments. | (8) |
| | c) | Define Q-factor. | (4) |

PART C

Answer any two full questions, each carries 20 marks.

- 7 a) Differentiate transducer from sensor. Explain various classification of transducer with examples. (10)
- b) Describe the working of Audio power meter with circuit diagram. (10)
- 8 a) What is the working principle of resistance transducer? Explain the working of strain gauge with neat sketch. (8)
- b) Describe the operation of proximity transducer with neat diagram. (6)
- c) Explain the block diagram of logic state analyser. (6)
- 9 a) List out any four specifications of digital voltmeter. (4)
- b) Explain the working principle of Hall effect transducer with neat diagram. (6)
- c) Explain the measurement of frequency using digital instrument with neat schematic. (10)
