

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
EIGHTH SEMESTER B.TECH DEGREE EXAMINATION, MAY 2019

Course Code: EC464
Course Name: LOW POWER VLSI DESIGN

Max. Marks: 100

Duration: 3 Hours

PART A

Answer any two full questions, each carries 15 marks.

Marks

- 1 a) What is threshold voltage of MOSFET? Write down the mathematical expression. (6)
What is the effect of body voltage on threshold voltage?
- b) Draw the energy band diagrams of MIS structure at different bias conditions. (9)
- 2 a) When MOSFET is considered as a short channel MOSFET? (3)
- b) What is Hot electron effect? Explain with diagram. (6)
- c) Derive an expression for short circuit power dissipation of a CMOS inverter. (6)
- 3 a) Explain the transistor leakage mechanisms of deep submicron transistors. (10)
- b) What is switching power dissipation and how it can be minimized? (5)

PART B

Answer any two full questions, each carries 15 marks.

- 4 a) What is Domino CMOS logic? What is its advantage? (5)
- b) Implement the function $Z = AB(C + D)(E + F)GH$ using three units of Domino CMOS logic. (10)
- 5 a) What are short channel effects? (5)
- b) How to minimize short channel effects? (10)
- 6 a) Explain the working of clocked CMOS circuits. (5)
- b) What is charge sharing in clocked CMOS circuits? How it can be overcome? (5)
- c) Implement the logic function $F = (PQ + RS + T)'$ using clocked CMOS logic. (5)

PART C

Answer any two full questions, each carries 20 marks.

- 7 a) Implement the function $F = (A'B + AB')$ using (16)
 1. Fully complementary logic
 2. Pass transistor Logic
 3. pseudo NMOS Logic

4. DCVS logic

- b) What are the advantages of DCVS logic over fully complementary logic? (4)
- 8 a) Draw and explain one stage adiabatic buffer. (7)
- b) Draw and explain the circuit of an adiabatic CMOS AND/NAND gate. (8)
- c) Briefly describe adiabatic switching. (5)
- 9 a) What is a pass transistor logic and complementary pass transistor logic? (10)
- What is the advantage of pass transistor logic?
- Why NMOS can pass only 'weak 1'?
- b) Implement $F = A+B$ and $F' = (A+B)'$ using pass transistor logic. (6)
- c) Explain the concept of pulsed power supplies (4)
